

CHAPTER 16

BASIC DIGITAL ELECTROHYDRAULIC DEVICES



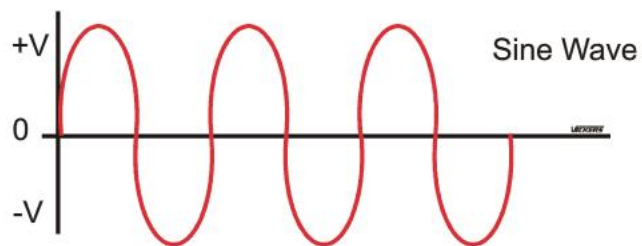


Figure 16-1 Sine wave

COPYRIGHT © (2001) EATON CORPORATION

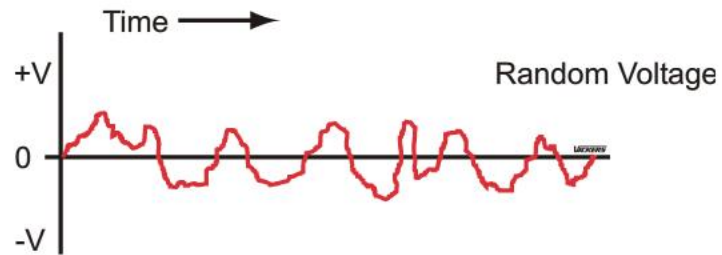


Figure 16-2 Random AC voltage

COPYRIGHT © (2001) EATON CORPORATION

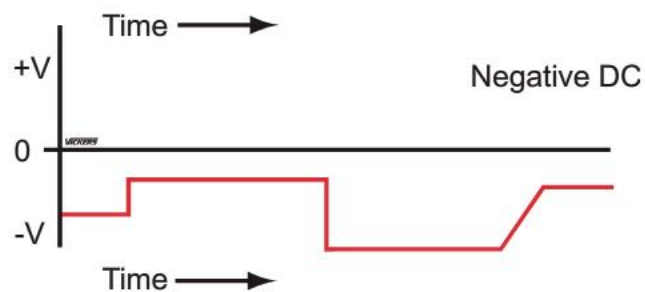


Figure 16-3 Varying negative DC voltage

COPYRIGHT © (2001) EATON CORPORATION

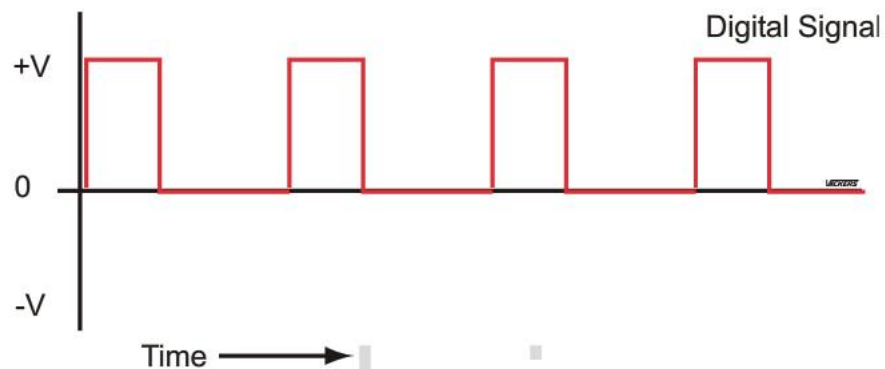


Figure 16-4 Digital signals.

COPYRIGHT © (2001) EATON CORPORATION

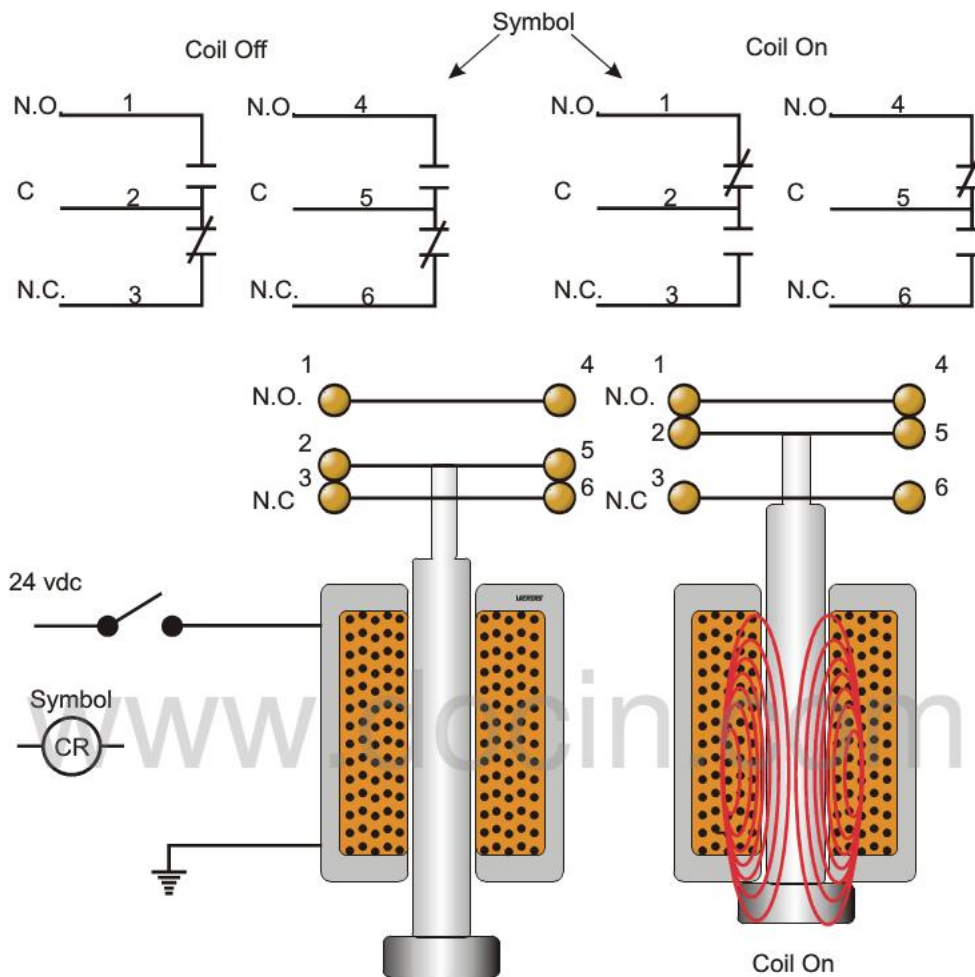


Figure 16-5 Basic relay construction

COPYRIGHT © (2001) EATON CORPORATION

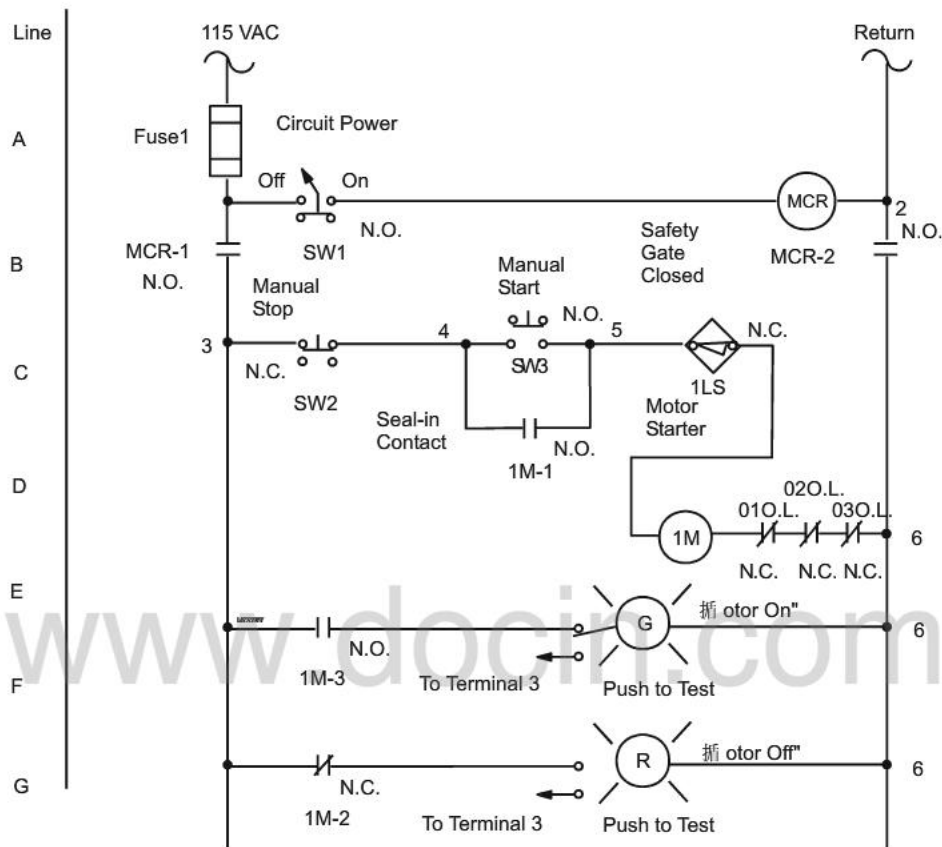


Figure 16-6 115 volt, single phase circuit is used to control a 480 volt, three-phase motor

COPYRIGHT © (2001) EATON CORPORATION

	RELAYS	MICROPROCESSORS
Speed	Slow response (milliseconds)	Fast response (microseconds)
Cost	\$50 and up	\$7.50 to \$20
Power Use	Watts	Milliwatts
Number of Components Required	Thousands of relays	= 1 microprocessor
Size	0.1 - 6 cubic inches	Less than 0.1 cubic inches
Flexibility	Single function	Hundreds of functions

Figure 16-7 Comparison between relays and microprocessors

COPYRIGHT © (2001) EATON CORPORATION

MEGERS


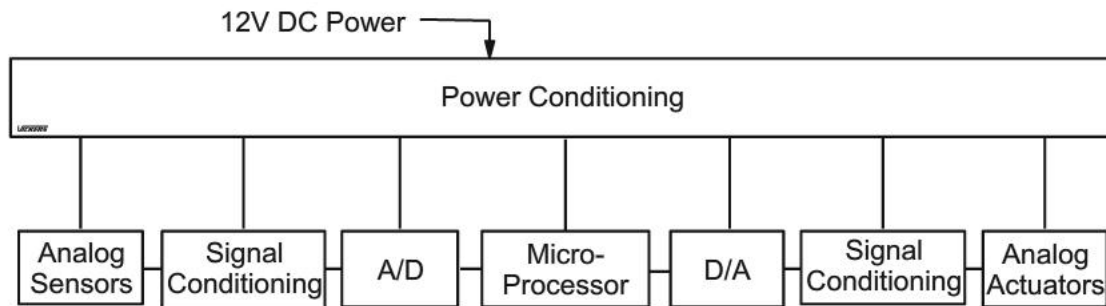


Figure 16-8 Block diagram of a microprocessor based electrohydraulic closed loop control system

COPYRIGHT © (2001) EATON CORPORATION

Programmable Logic Controller

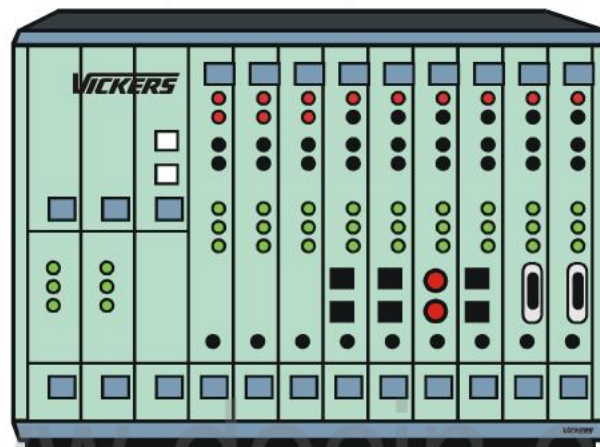

Processing
Unit
(CPU)

Input and Output modules

Figure 16-9 Programming logic controller

COPYRIGHT © (2001) EATON CORPORATION

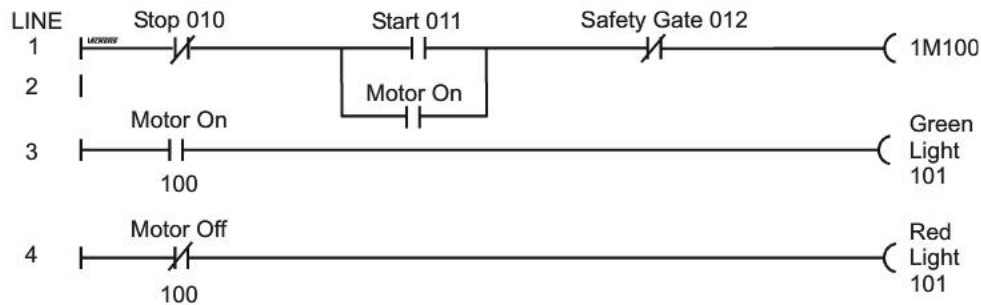


Figure 16-10 PLC ladder diagram for relay logic circuit

COPYRIGHT © (2001) EATON CORPORATION

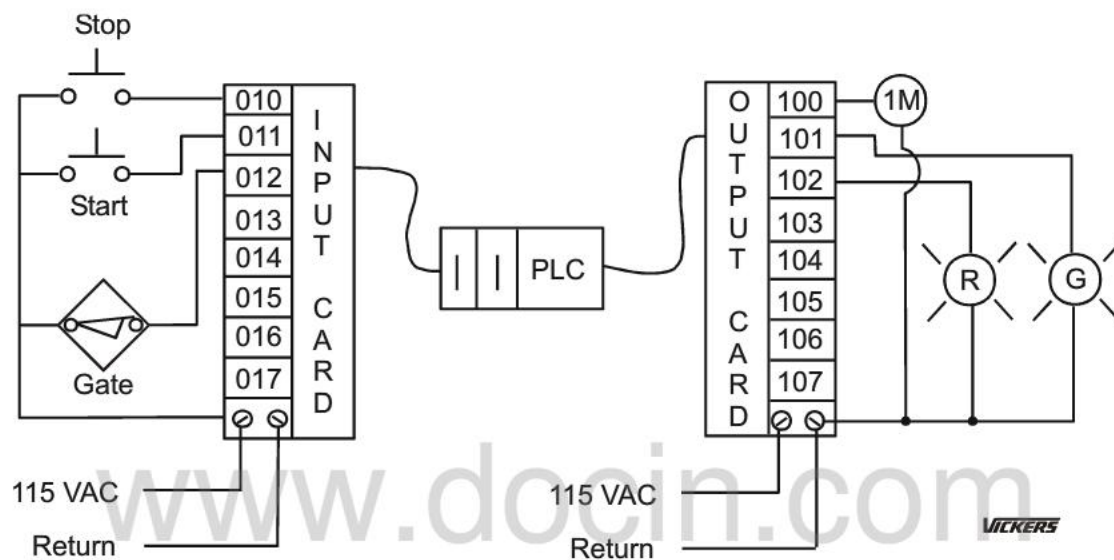


Figure 16-11 PLC wiring diagram for relay logic circuit

COPYRIGHT © (2001) EATON CORPORATION

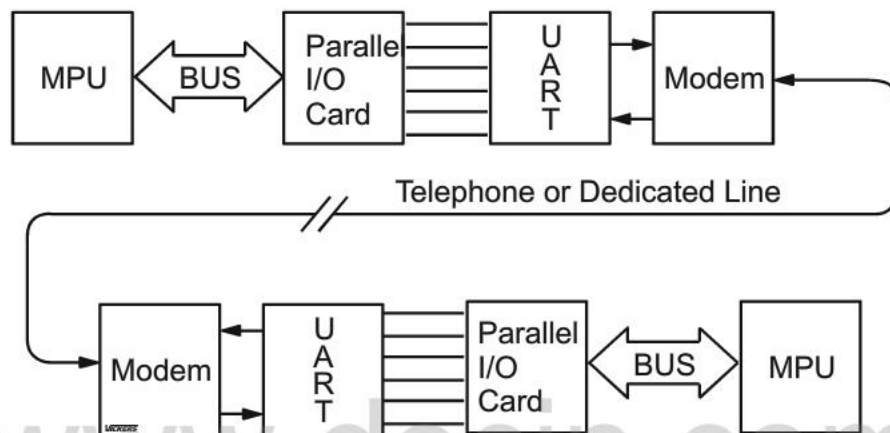


Figure 16-12 Modem used for data transmission

COPYRIGHT © (2001) EATON CORPORATION

Serial transmission of digital byte 10101110_2

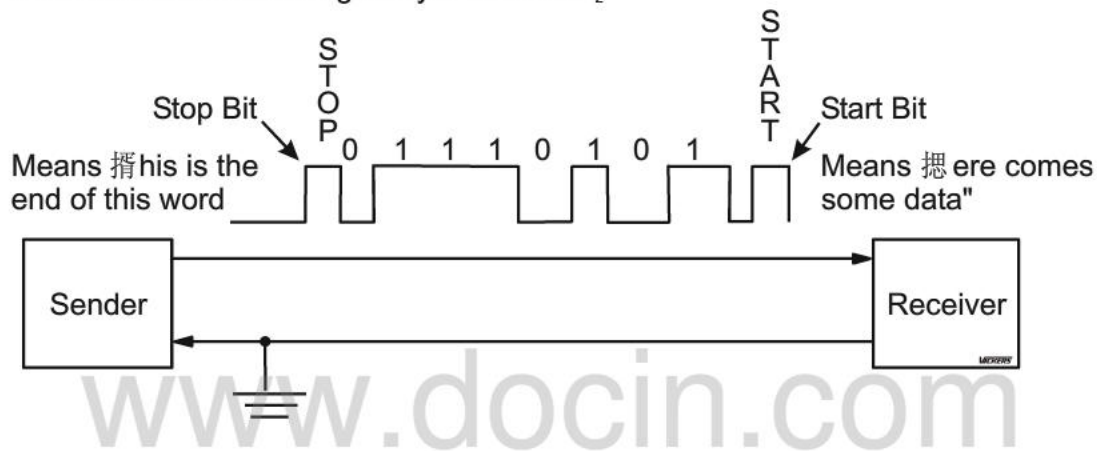


Figure 16-13 Serial data transmission

COPYRIGHT © (2001) EATON CORPORATION


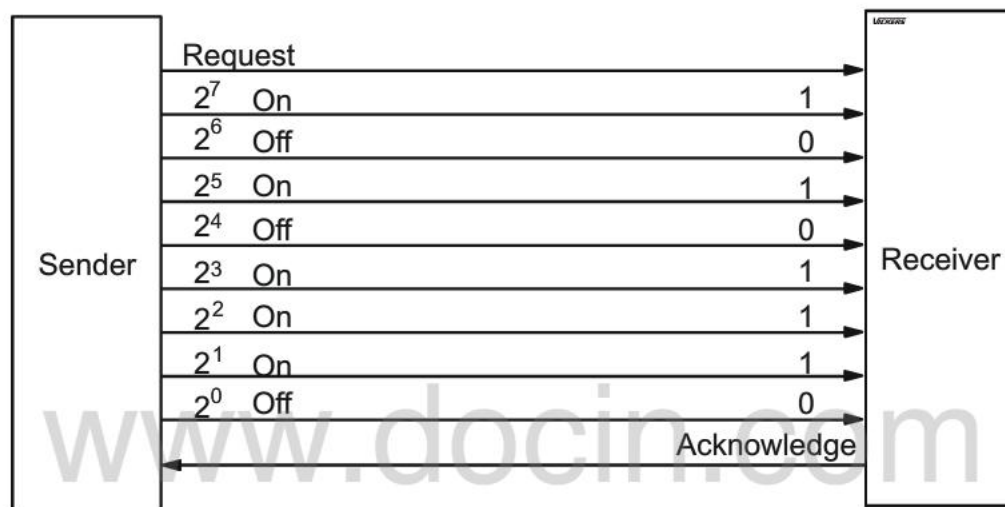


Figure 16-14 Parallel transmission data


COPYRIGHT © (2001) EATON CORPORATION

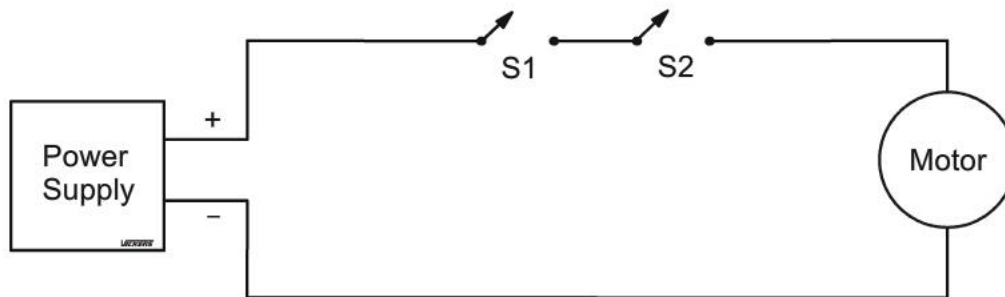

Both S1 and S2 must be closed before motor can run

Figure 16-15 Simple electrical AND circuit

COPYRIGHT © (2001) EATON CORPORATION

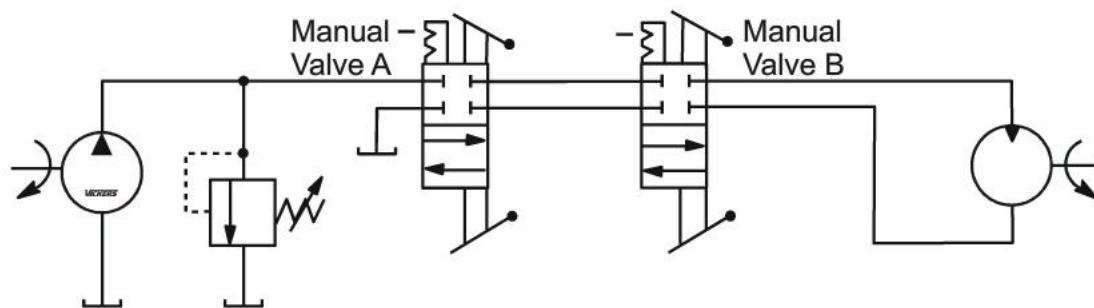

Hydraulic equivalent 挡ND" circuit. Both valves must be opened to run motor

Figure 16-16 Simple hydraulic equivalent of AND control

COPYRIGHT © (2001) EATON CORPORATION


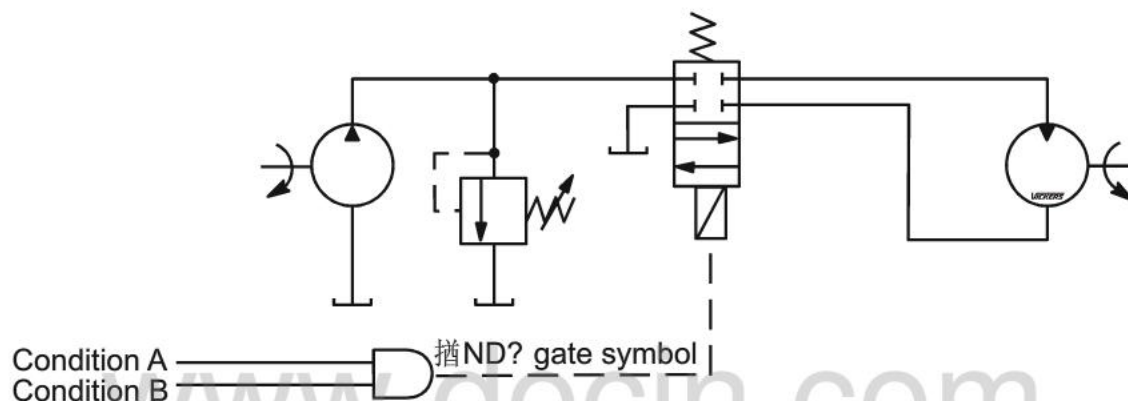


Figure 16-17 Digital AND circuit


COPYRIGHT © (2001) EATON CORPORATION

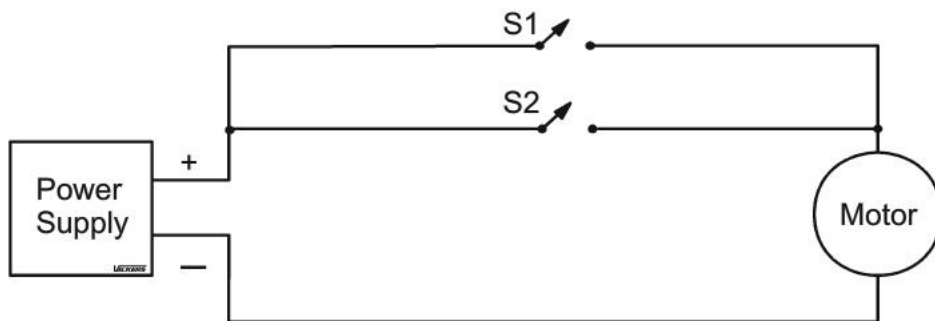

Either S1 OR S2 must be closed before motor can run

Figure 16-18 Simple electrical OR circuit

COPYRIGHT © (2001) EATON CORPORATION

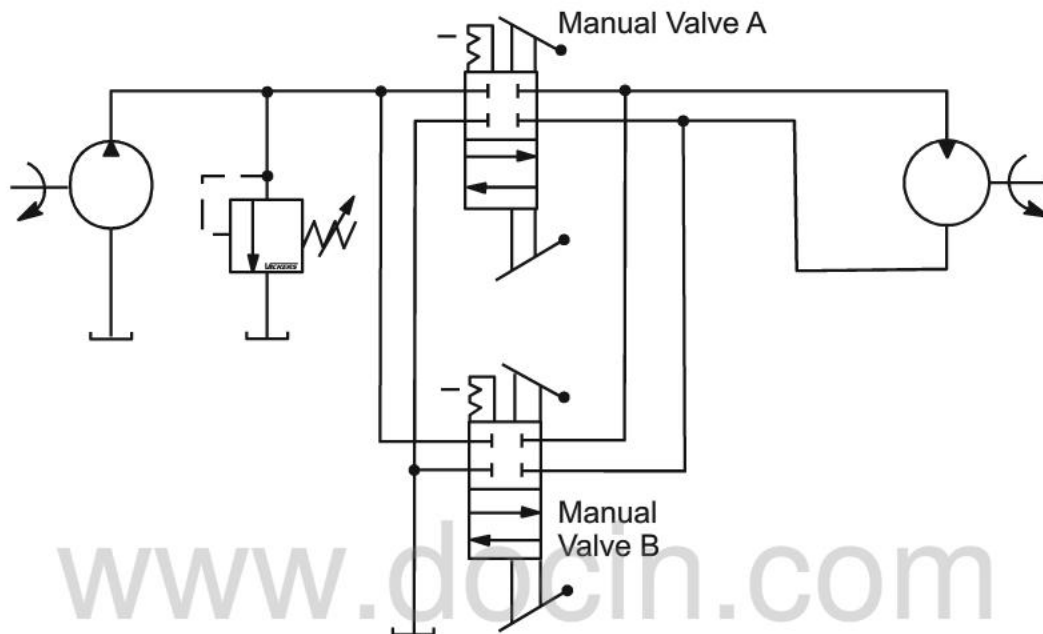

Hydraulic equivalent 搞 R? circuit. Either valve A or B must be opened to run motor

Figure 16-19 Simple Hydraulic equivalent OR circuit

COPYRIGHT © (2001) EATON CORPORATION


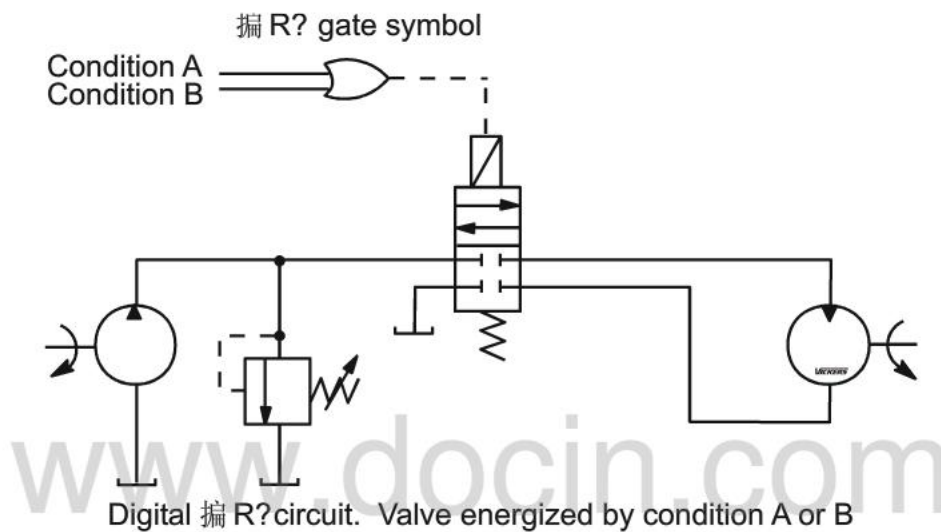


Figure 16-20 Digital OR circuit

COPYRIGHT © (2001) EATON CORPORATION

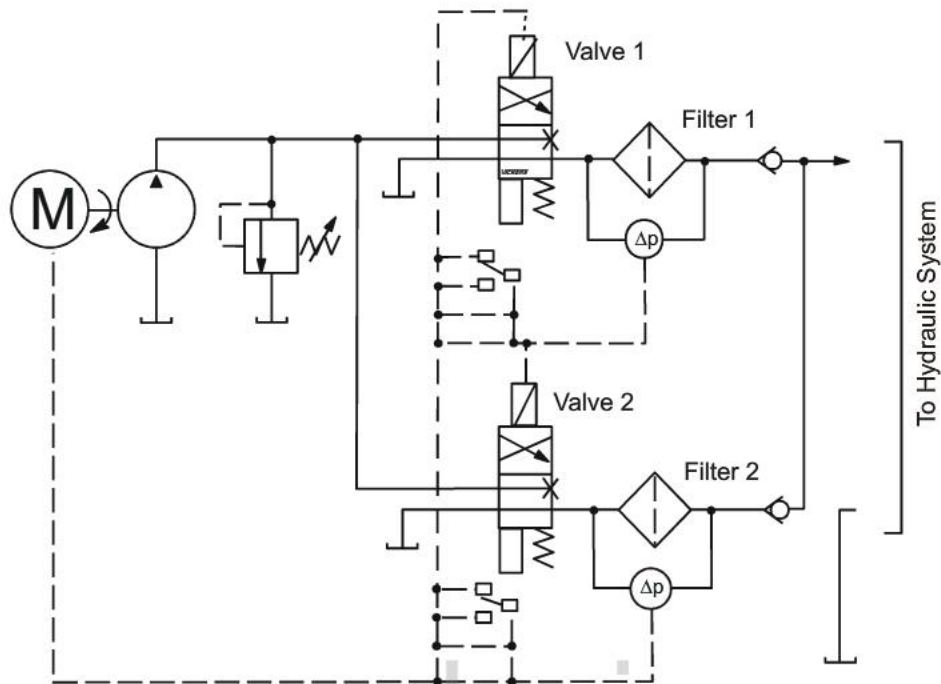

Δp = Differential Pressure Switch. Normal condition = Clean Filter = Low Differential Pressure
Contacts time delayed to avoid triggering due to pressure surges.

Valves 1 and 2 are = Solenoid operated, spring offset with monitor switch.
Switch off = Valve off = Oil flow to filter off.

The above circuit will be interlocked to automatically switch to a clean filter and to shut down the motor if both filters are dirty.

Figure 16-21 Machine interlock circuit

COPYRIGHT © (2001) EATON HYDRAULICS

MEGABIT

DECIMAL	BINARY
0	0000
1	0001
2	0010
3	0011
4	0100
5	0101
6	0110
7	0111
8	1000
9	1001
10	1010
11	1011
12	1100
13	1101
14	1110
15	1111

Figure 16-23 Binary and decimal equivalents

COPYRIGHT © (2001) EATON CORPORATION

DECIMAL NUMBER

3,240,897₁₀ Denotes base of
number system

DIGIT	3	2	4	0	8	9	7
POSITION	7	6	5	4	3	2	1
WEIGHT	10 ⁶	10 ⁵	10 ⁴	10 ³	10 ²	10 ¹	10 ⁰
VALUE	3,000,000	200,000	40,000	0	800	90	7


BINARY NUMBER

MSB 1101101₂ LSB

DIGIT	1	1	0	1	1	0	1
POSITION	7	6	5	4	3	2	1
WEIGHT	2 ⁶	2 ⁵	2 ⁴	2 ³	2 ²	2 ¹	2 ⁰
VALUE	64	32	16	8	4	2	1

Figure 16-24 Bit positions values

COPYRIGHT © (2001) EATON CORPORATION

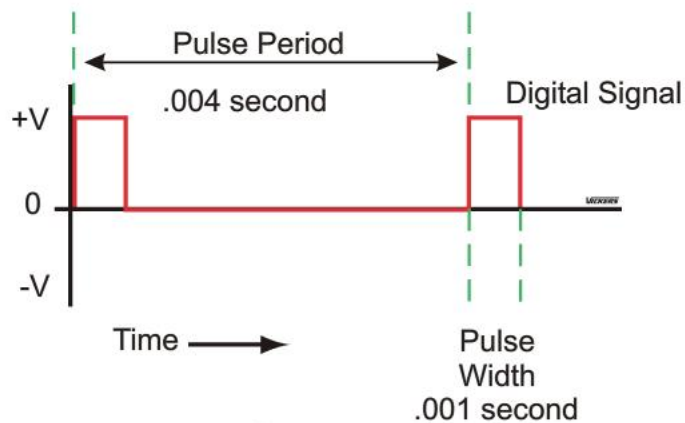

$$\text{Frequency} = \frac{\# \text{ of pulses}}{\text{Period of pulses}} = \frac{1 \text{ pulse}}{.004 \text{ second}} = 250 \text{ pulses/sec} = 250 \text{ Hz}$$

Figure 16-25 Relationship between pulse width and frequency

COPYRIGHT © (2001) EATON CORPORATION

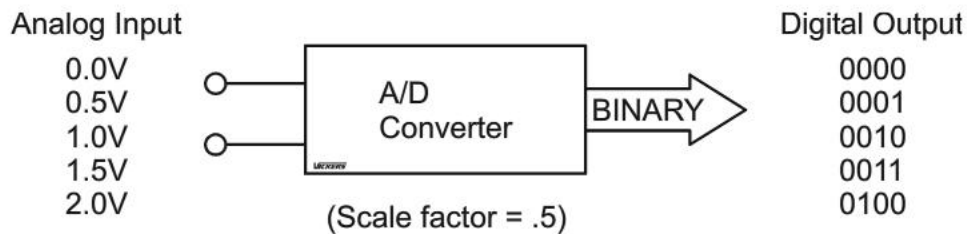


Figure 16-26 Analog-to-Digital converter

COPYRIGHT © (2001) EATON CORPORATION



Figure 16-27 Digital-to-Analog Converter

COPYRIGHT © (2001) EATON CORPORATION