

CHAPTER 9

BASIC ELECTRICAL PRINCIPLES AND OPERATIONAL AMPLIFIERS




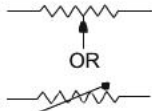

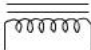

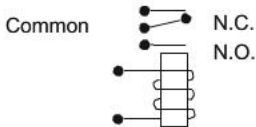
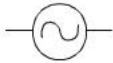
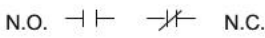

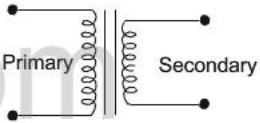


Conductor, Connected		Resistor, Variable	
Conductors, Not Connected		Solenoid Coil, Iron Core	
Battery, Dry Cell or DC Source		Relay	
AC Source		Relay Contacts	
AC Power Plug		Transformer, Iron Core	
Fuse		Diode	

Figure 9-1 Common electrical schematic symbols


















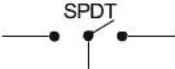


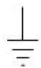




Lamp		Ammeter	
Switch Single Pole, Single Throw		Voltmeter	
Switch Single Pole, Double Throw		Ohmmeter	
Capacitor		Earth Ground	
Resistor, Fixed		Chassis Ground	
Resistor, Tapped			

Figure 9-1 Common electrical schematic symbols (continued)

ELECTRICAL		HYDRAULIC	
Resistor		Restriction	
Power Supply		Pump	
Capacitor		Double Spring Loaded Piston or Accumulator	
Switch		Directional Valve	
Diode		Check Valve	
Transformer		Intensifier	
Ground		Tank	

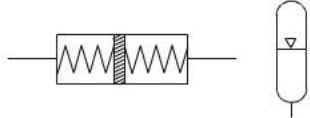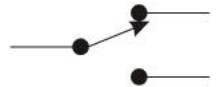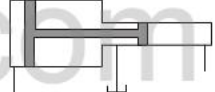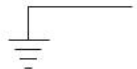VICKERS

Figure 9-2 Functional equivalence of electrical and hydraulic components

COPYRIGHT © (2001) EATON CORPORATION



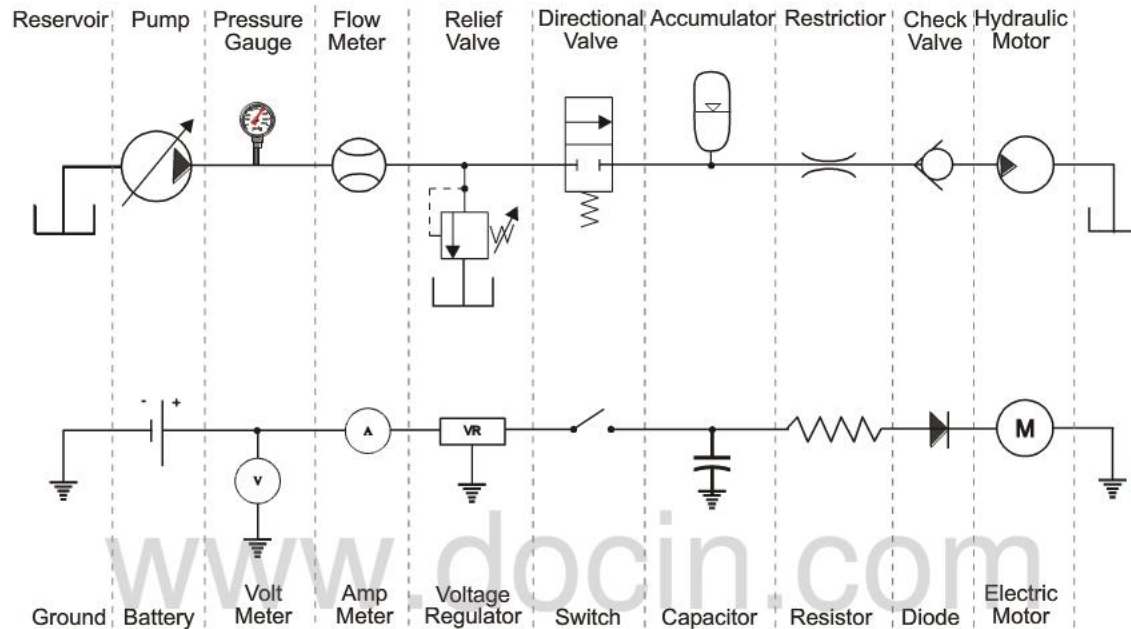


Figure 9-3 Comparison of simple hydraulic and electrical circuits

COPYRIGHT © (2001) EATON CORPORATION

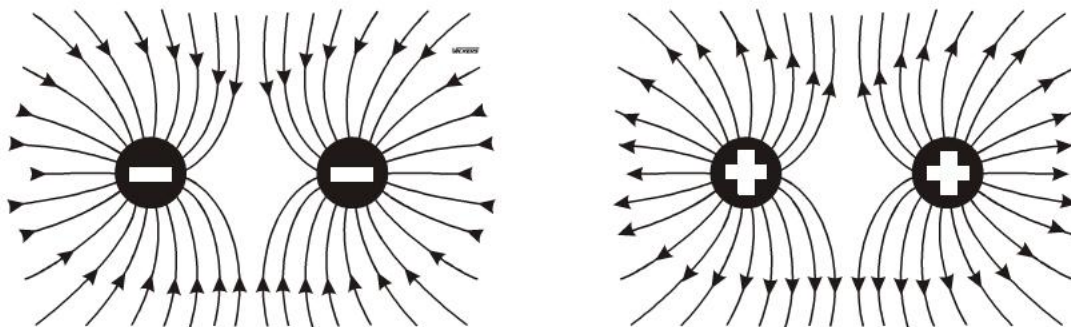

Like Charges Repel

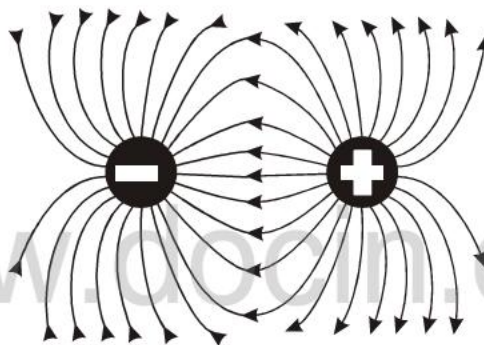

Unlike Charges Attract


Figure 9-4 The law of electrical charges

COPYRIGHT © (2001) EATONCORPORATION

1. With no external force applied, charges drift randomly within a conductor



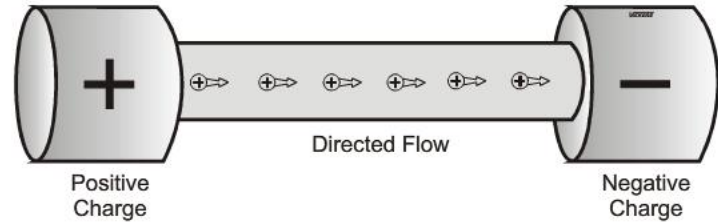2. When external force is applied, the flow of charges can be directed



3. Conventional current flows from positive to negative in a circuit

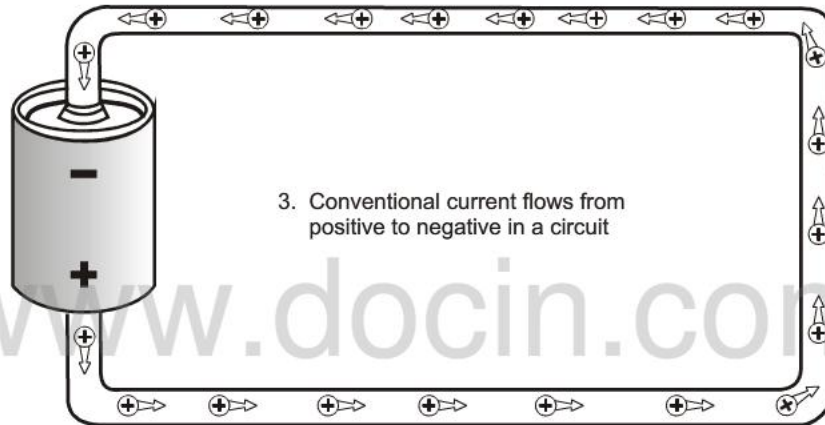


Figure 9-5 Conventional current flow

A. Current Flows in a Closed Circuit

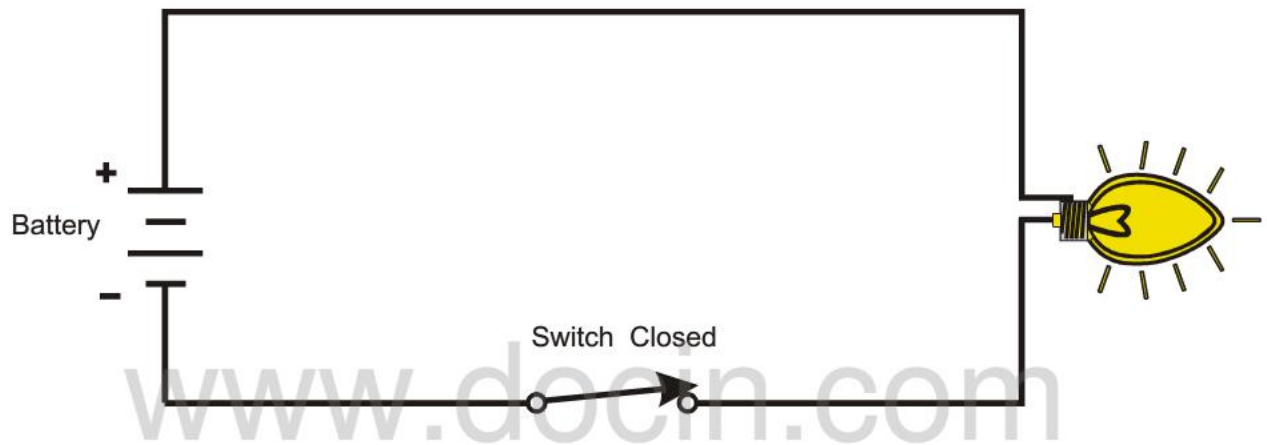


Figure 9-6 Closed and open circuits

COPYRIGHT © (2001) EATON CORPORATION

B. Current Cannot Flow in an Open Circuit

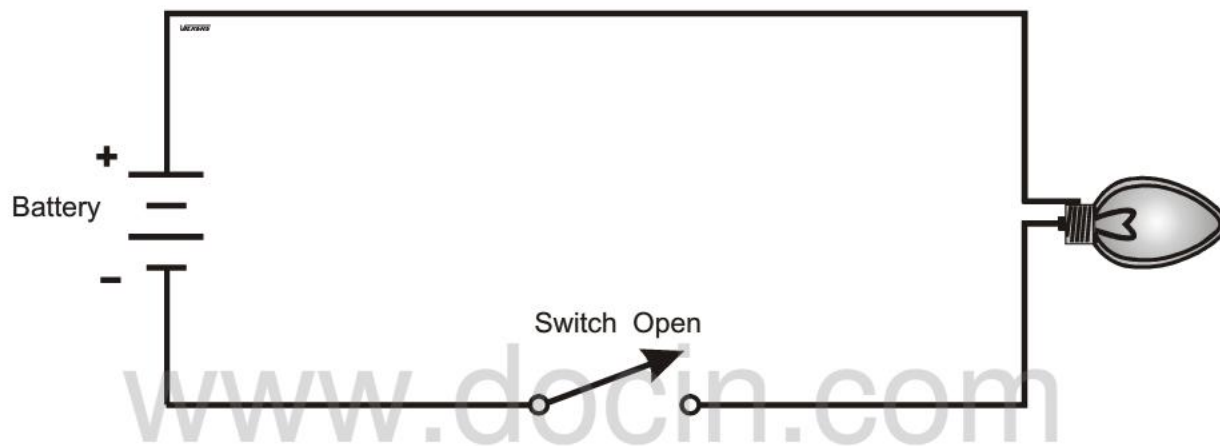


Figure 9-6 Closed and open circuits

COPYRIGHT © (2001) EATON CORPORATION

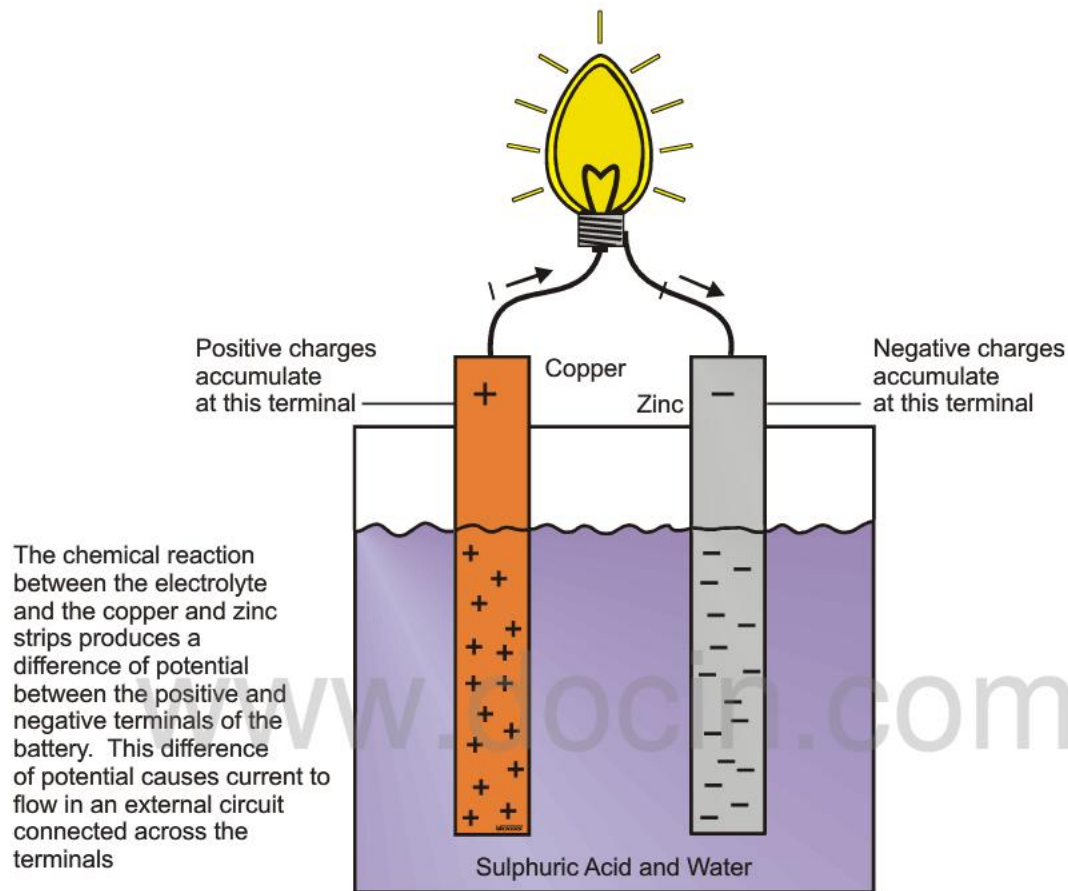


Figure 9-7 Battery as a power source

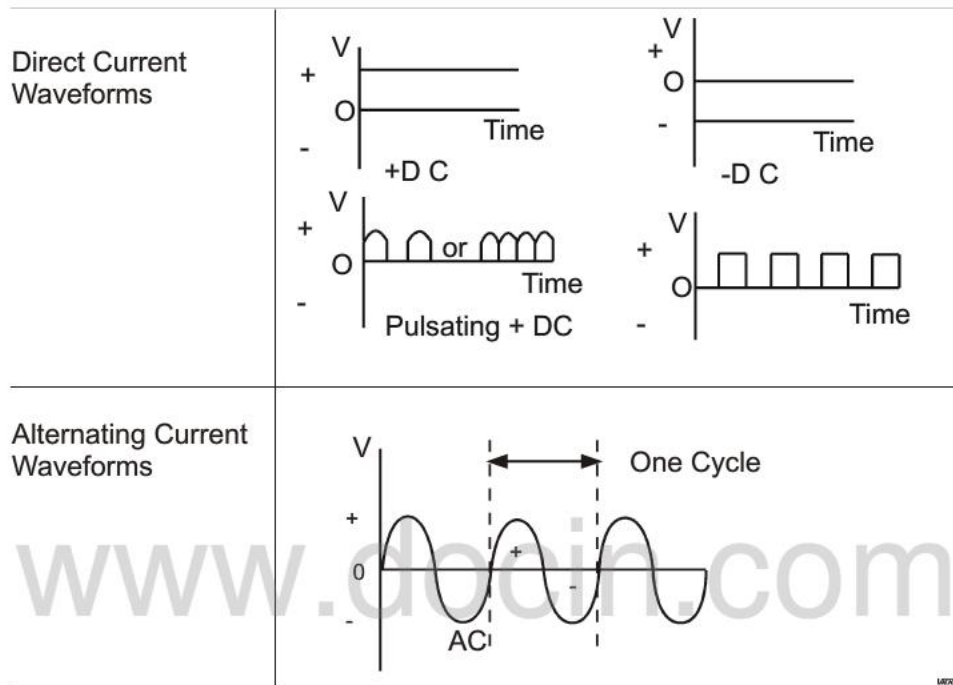

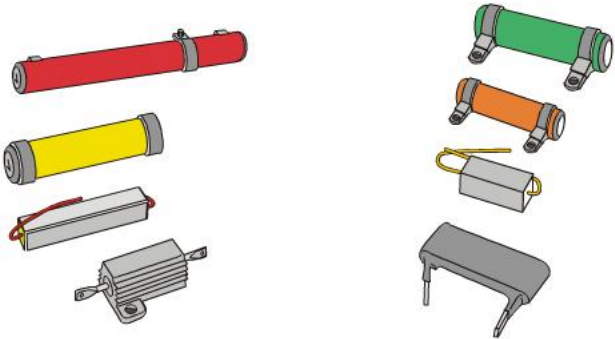
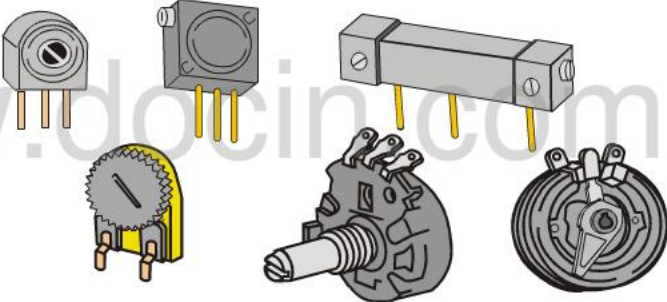


Figure 9-8 DC and AC waveforms

COPYRIGHT © (2001) EATON CORPORATION

<p>Typical Low Power Resistors (Fixed)</p>	
<p>Typical High Power Resistor (Fixed)</p>	
<p>Typical Variable Resistors</p>	

VICKERS

Figure 9-9 Fixed and variable resistors

COPYRIGHT © (2001) EATON CORPORATION



Figure 9-10 Analog meter


COPYRIGHT © (2001) EATON CORPORATION




Figure 9-11 Digital meter

COPYRIGHT © (2001) EATON CORPORATION

Remove power from circuit to be tested

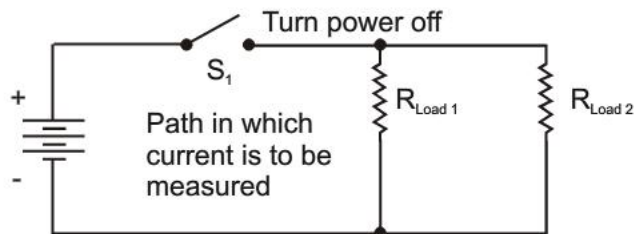

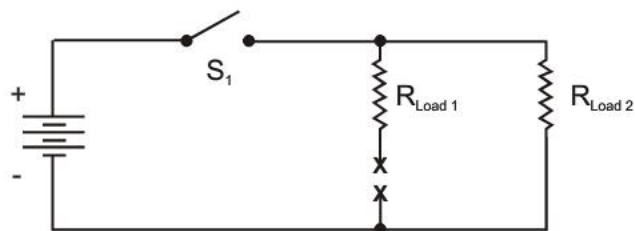Break the circuit at point where current is to be measured



Connect the ammeter in series with the circuit. Observe polarity. Then turn on the circuit power and measure the current flow


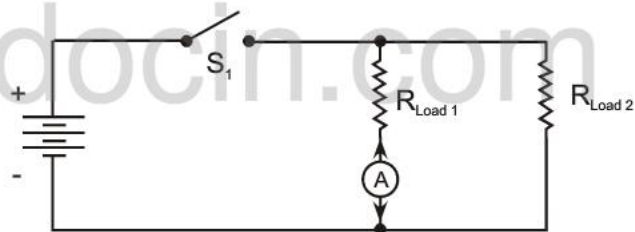


Figure 9-12 Series connection of ammeter

COPYRIGHT © (2001) EATON CORPORATION

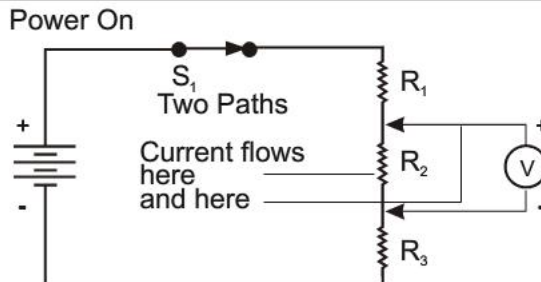A. Voltmeter Measuring A Voltage Drop

Voltmeter connected in parallel with circuit by touching test leads to each side of component. Meter reads voltage drop if current flows in circuit



B. Voltmeter Measuring A Voltage Rise

Voltmeter measures voltage rise even though no current is flowing in circuit. Voltmeter provides a path across positive and negative terminals of power source

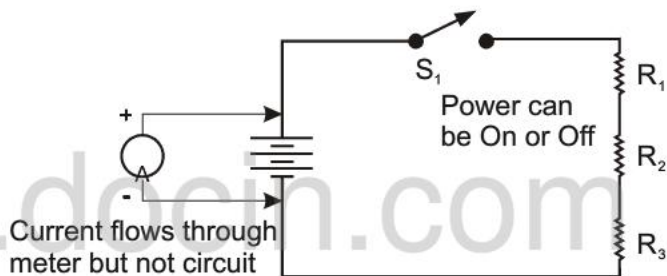


Figure 9-13 Voltmeter measuring voltage drop and voltage rise

COPYRIGHT © (2001) EATON CORPORATION

Voltmeter cannot measure voltage drop if current is not flowing in the circuit


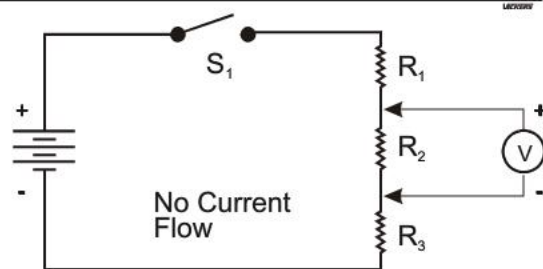


Figure 9-14 Voltmeter across component with no current flowing

COPYRIGHT © (2001) EATON CORPORATION

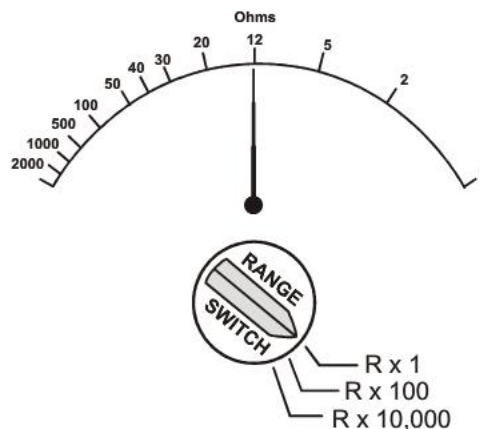After zero adjusting the meter and connecting the component between the test probes, the meter pointer indicates 12 on the Ohms scale. Since the range switch is set to R x 1, the resistance equals $12 \times 1 = 12$ Ohms



In this measurement, the meter pointer indicates 12, but the range switch is set to R x 100. The resistance being measured equals $12 \times 100 = 1200$ Ohms


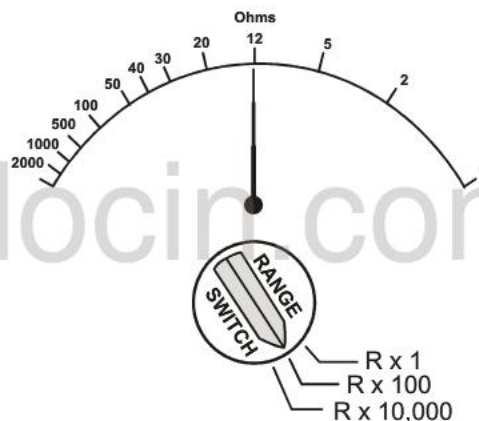


Figure 9-15 Ohmmeter measurements

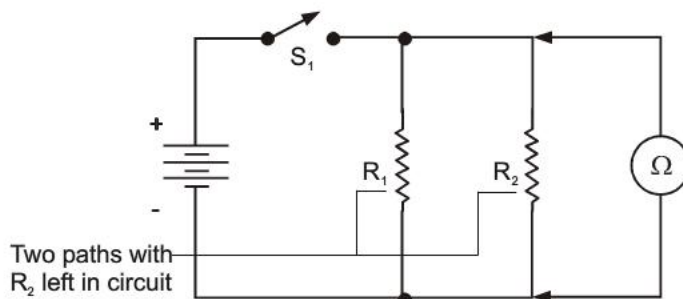When connecting an ohmmeter across a component (R_2) a false reading will be obtained if the component is not disconnected from the circuit. When the ohmmeter is connected as shown, meter current can flow through both R_2 and R_1 . The measurement will be a combination of R_1 and R_2 values resulting in a false reading - lower than expected



When the component to be measured with the ohmmeter is disconnected from the circuit, meter current has only one path it can follow. This allows a true measurement of the component with the ohmmeter

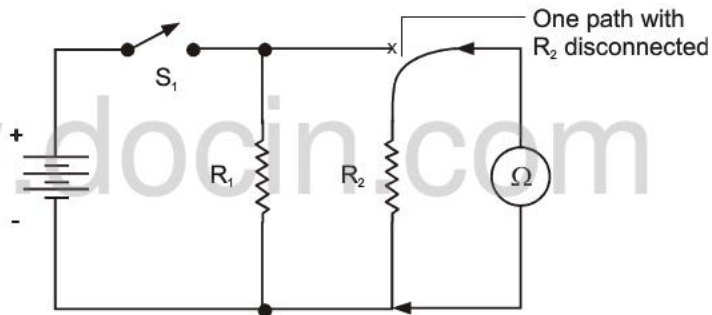


Figure 9-16 False ohmmeter readings


A. Simple Flashlight Circuit

Use Ohm's Law to solve for I:

$$I = E/R = 6V/120W = 0.05A$$

Convert A to mA:

$$0.05A \times 1000 = 50 \text{ mA}$$

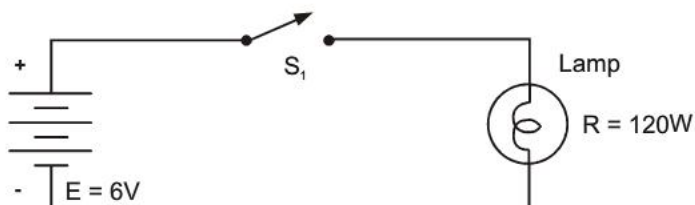


B. Voltage Increased (to 12V)

Voltage has been doubled. According to Ohm's Law, the current should also be doubled (direct relationship).

$$I = E/R = 12V/120W = 0.1A$$

$$0.1A \times 1000 = 100 \text{ mA}$$

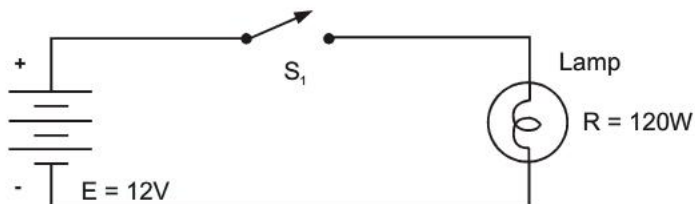


C. Resistance Increased (to 240W)

Resistance has been doubled. According to Ohm's Law, the current should also be halved (inverse relationship).

$$I = E/R = 12V/240W = 0.05A$$

$$0.05A \times 1000 = 50 \text{ mA}$$

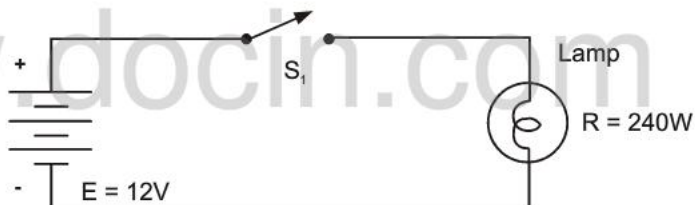

MEKERS

Figure 9-17 Ohm's law proof


CIRCUIT ELEMENT	DEFINITION	UNIT OF MEASUREMENT	UNIT SYMBOL	MEASURED WITH	FUNCTION SWITCH POSITION	OHM 欧姆 OR WATT 瓦T LAW
Current	The flow of electrons from + to - around a circuit	Amperes (amps)	A	Ammeter	ACmA or DCmA	$I = E / R$ $I = P / E$ $I = \sqrt{P/R}$
Voltage (EMF)	The force which causes current to flow	Volts	V	Voltmeter	ACV or DCV	$E = I \times P$ $E = P / I$ $E = \sqrt{P/R}$
Resistance	The opposition to current flow	Ohms	W	Ohmmeter	Ohms	$R = E / I$ $R = E^2 / P$ $R = P / I^2$
Power	The rate of doing electrical work	Watts	W	Wattmeter or Calculated	N/A	$P = I \times E$ $P = I^2 R$ $P = E^2 / R$

Figure 9-18 Electrical circuit element summary chart

COPYRIGHT © (2001) EATON CORPORATION

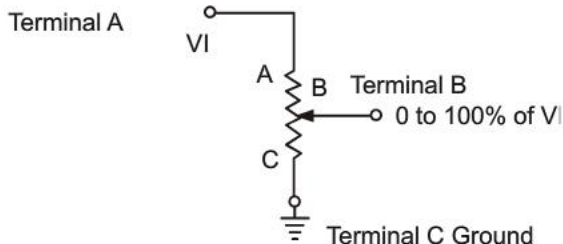
A. Attenuator Circuit

The voltage available at terminal B is some percentage of the input voltage (V_I). The exact percentage (from 0 to 100) depends on the potentiometer setting



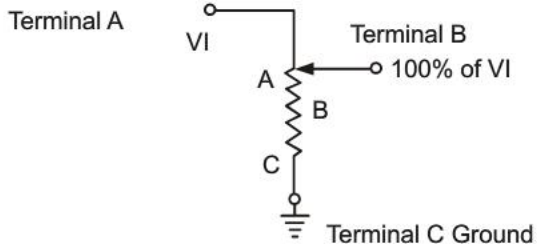B. Attenuator set for 100% of Input

Current flow bypasses resistance if attenuator is adjusted for minimum attenuation. Terminal B is electrically connected to terminal A



C. Attenuator set for 0% of Input

Current flow bypasses resistance if attenuator is adjusted for minimum attenuation. Terminal B is electrically connected to terminal A

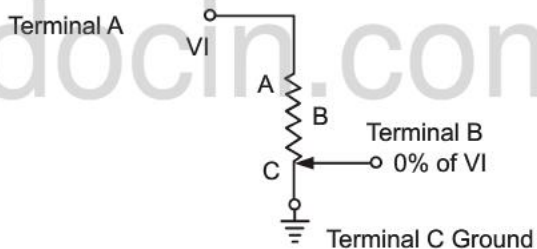


Figure 9-19 Potentiometer operation

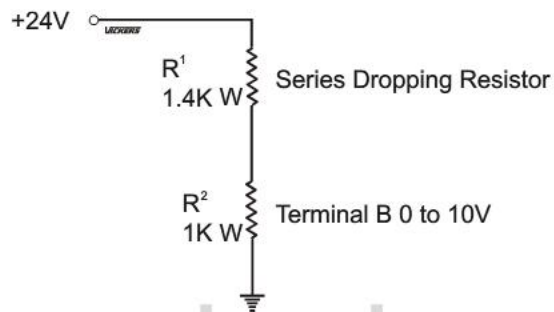


Figure 9-20 Potentiometer with series dropping resistor

COPYRIGHT © (2001) EATON CORPORATION

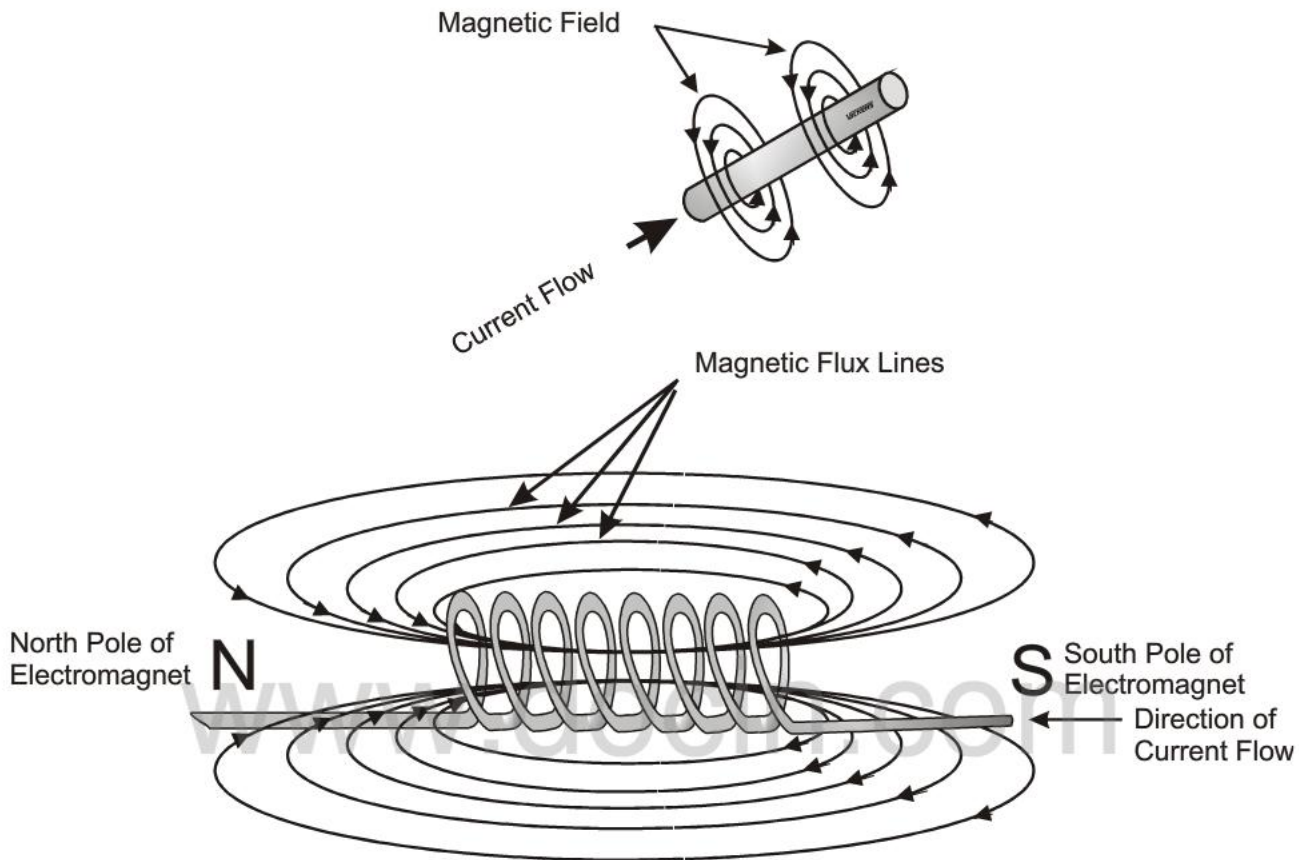


Figure 9-21 Magnetic field around solenoid coil

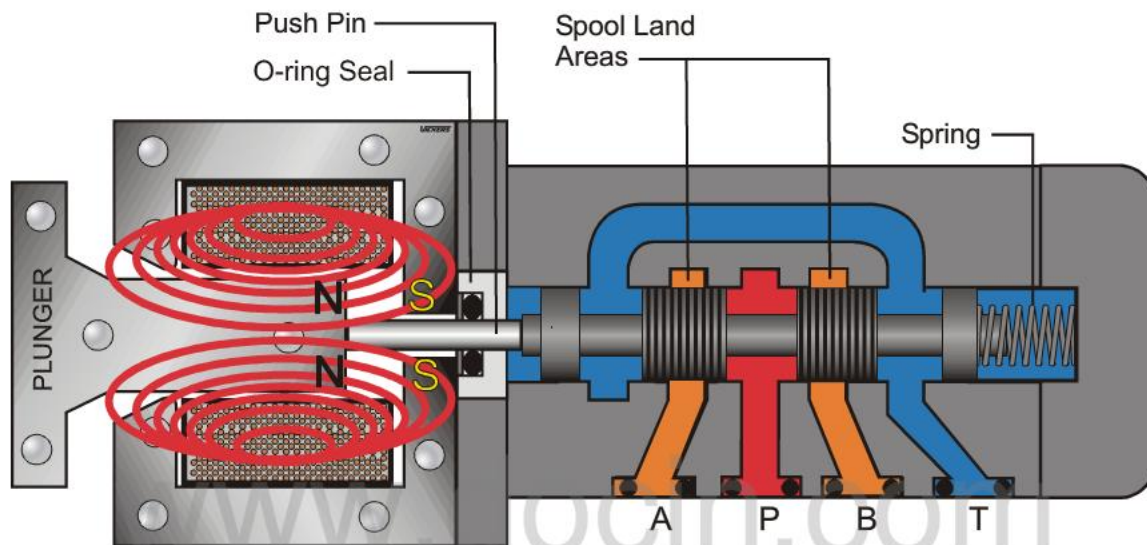


Figure 9-22 Air gap solenoid construction

COPYRIGHT © (2001) EATON CORPORATION

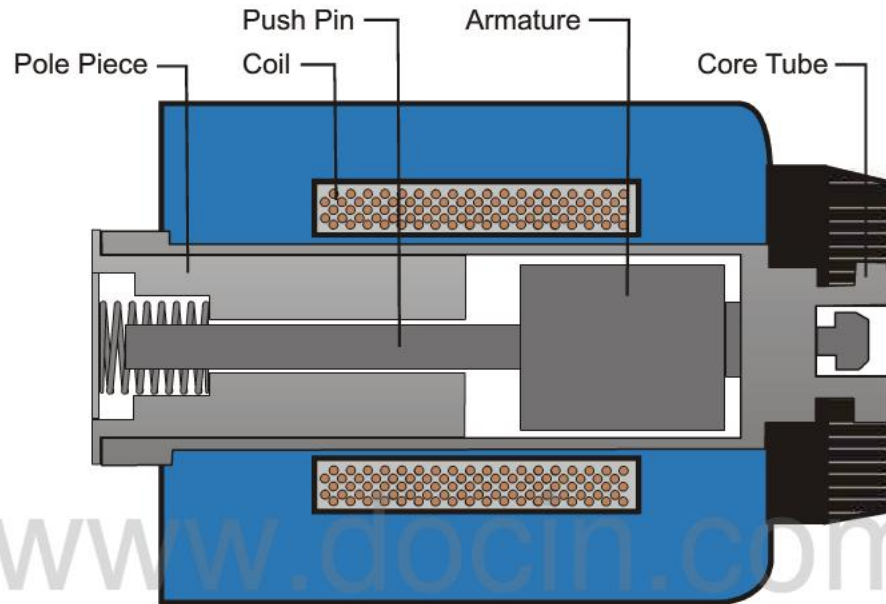


Figure 9-23 Wet armature solenoid construction

COPYRIGHT © (2001) EATON CORPORATION

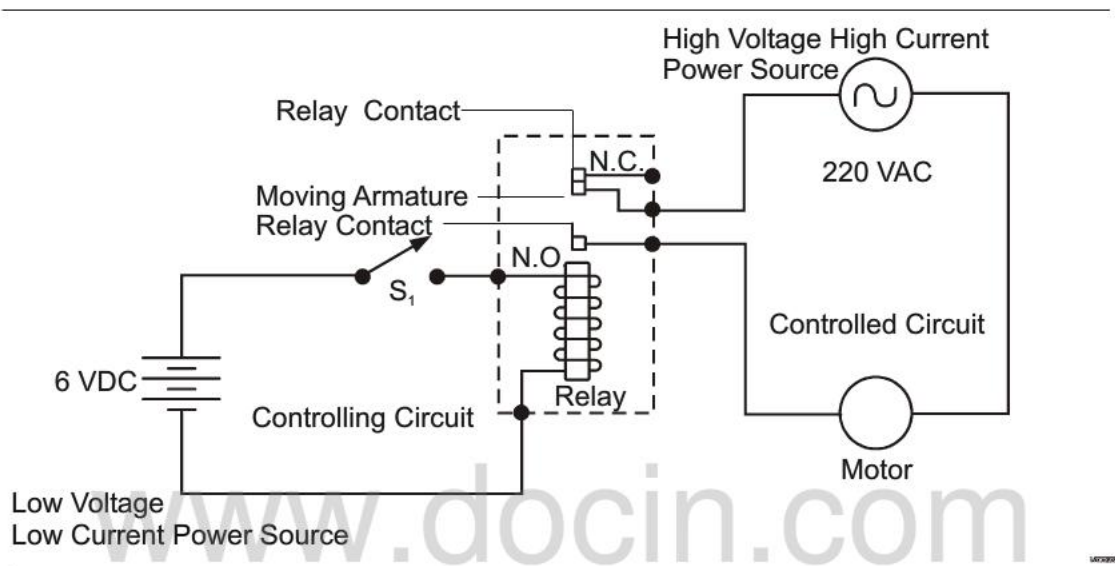


Figure 9-24 Simple relay circuit

COPYRIGHT © (2001) EATON CORPORATION

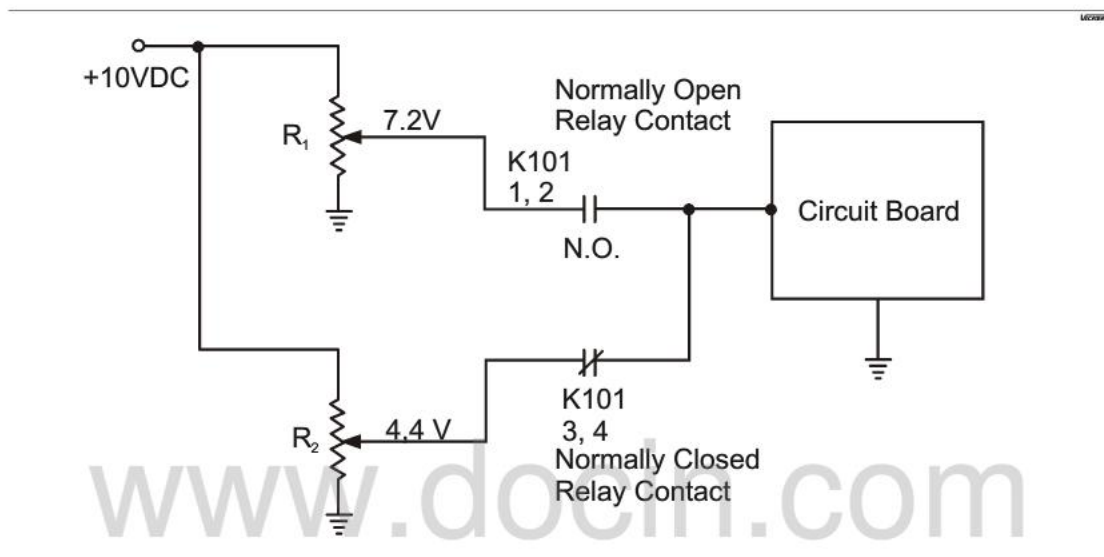


Figure 9-25 Relay controlling two input voltages

COPYRIGHT © (2001) EATON CORPORATION

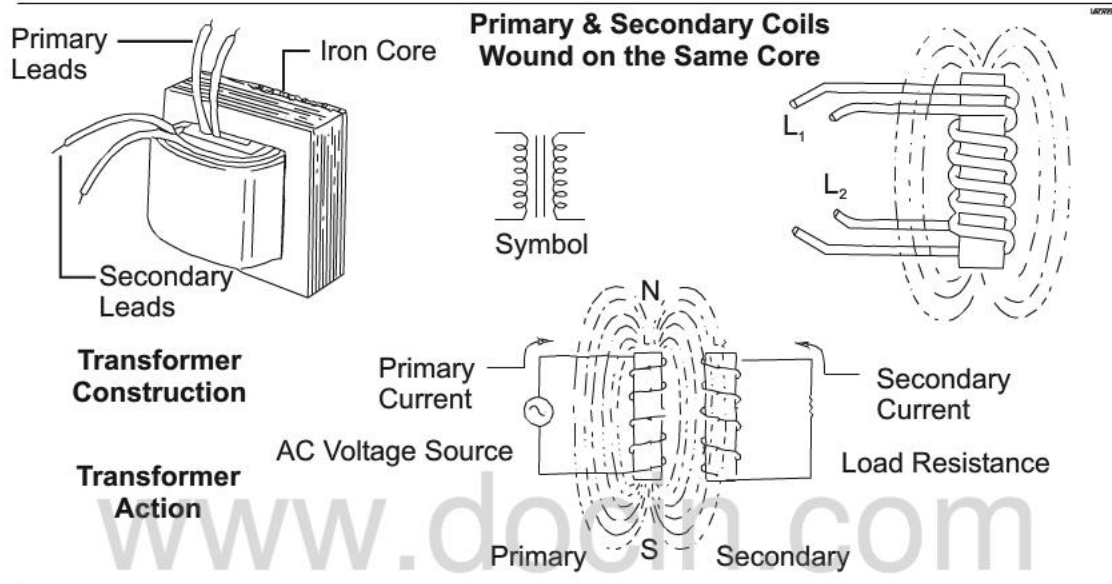


Figure 9-26 Iron core transformer

COPYRIGHT © (2001) EATON CORPORATION

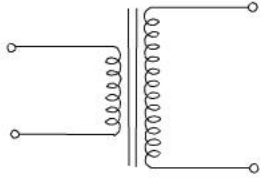
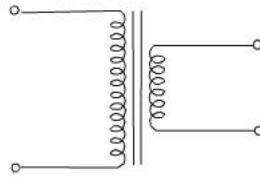
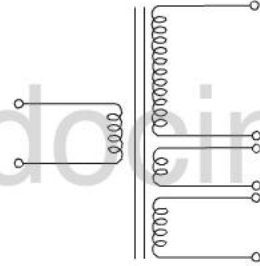
A. Step-Up Transformer Turns = 1000 E = 115V I = 4A P = 460W		Secondary Turns = 2000 E = 230V I = 2A P = 460W
B. Step-Down Transformer Turns = 800 E = 120V I = 1A P = 120W		Secondary Turns = 200 E = 30V I = 4A P = 120W
C. Transformer With Three Secondaries Turns = 800 E = 120V I = 1A P = 120W		Secondary 1 Turns = 1600 Secondary 2 Turns = 400 Secondary 3 Turns = 800

Figure 9-27 Transformer types

COPYRIGHT © (2001) EATON CORPORATION


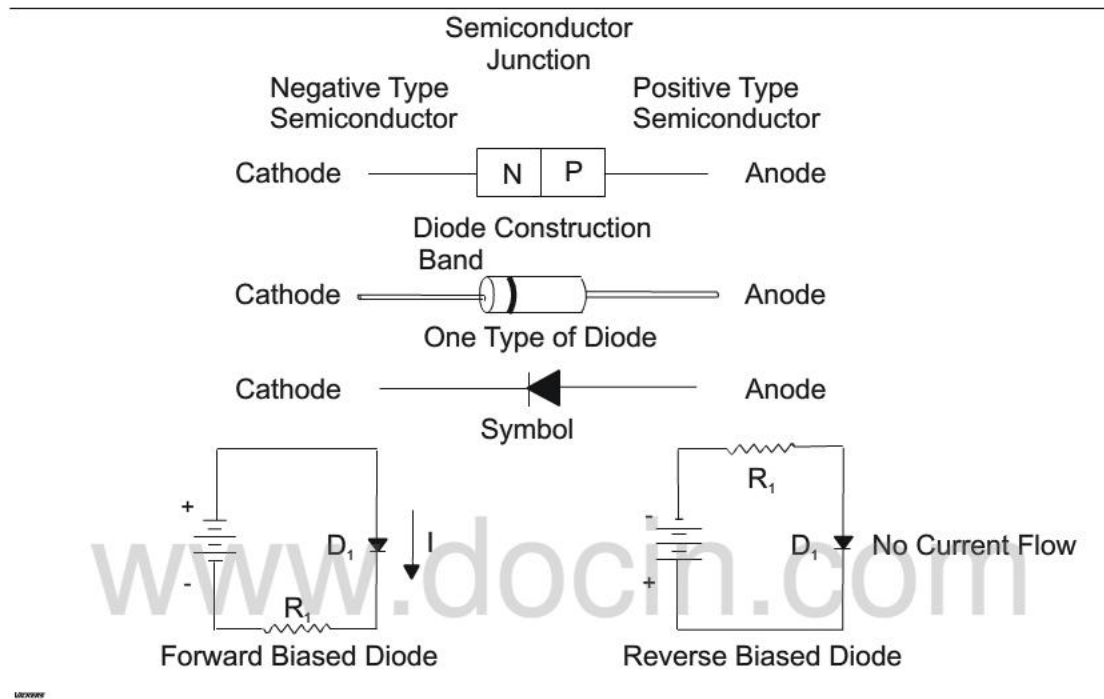


Figure 9-28 Semiconductor diode

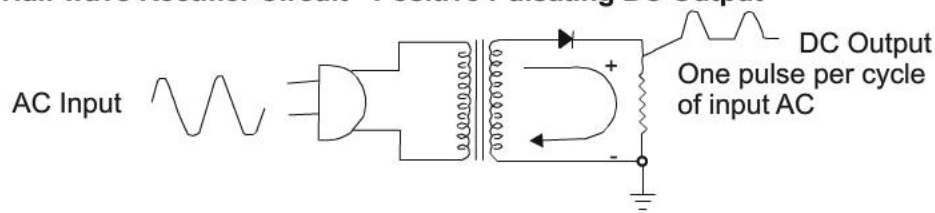A. Half wave Rectifier Circuit - Positive Pulsating DC Output



B. Half wave Rectifier Circuit - Negative Pulsating DC Output

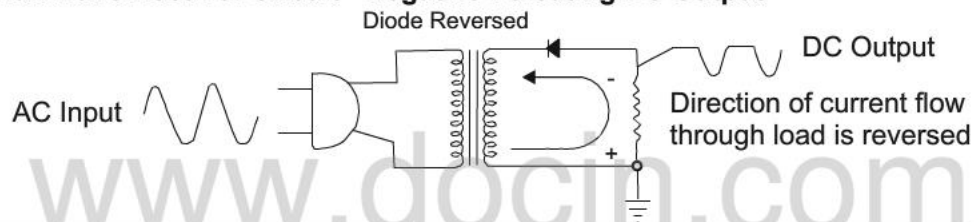


Figure 9-29 Half wave rectifier circuits

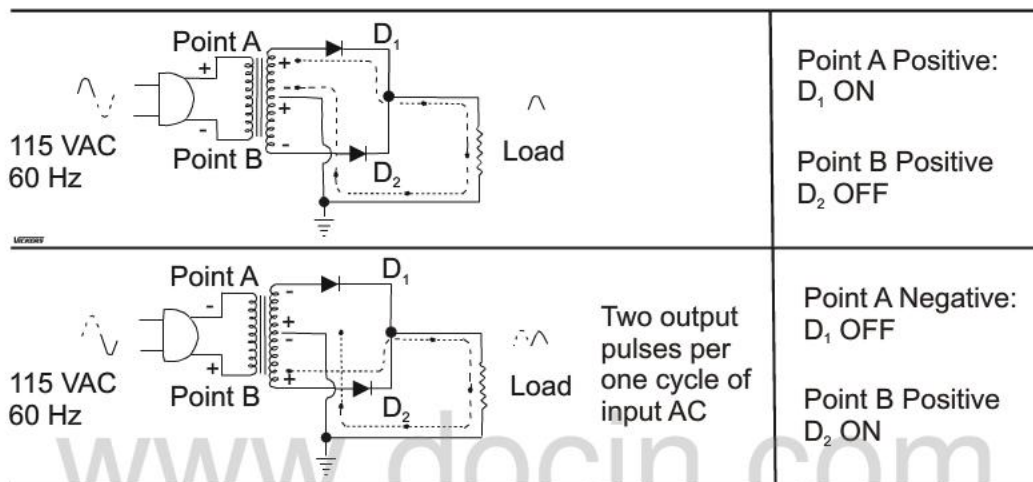


Figure 9-30 Full wave rectifier circuit operation

COPYRIGHT © (2001) EATON CORPORATION

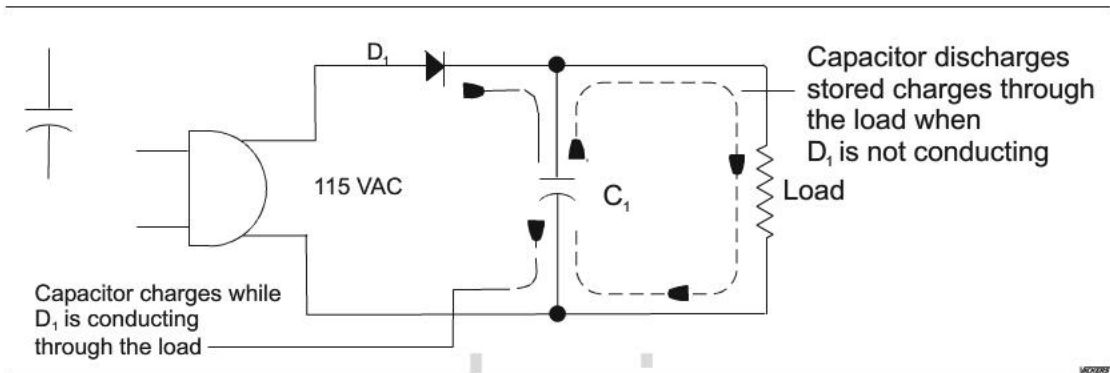


Figure 9-31 Capacitor used as filter for rectifier circuit

COPYRIGHT © (2001) EATON CORPORATION

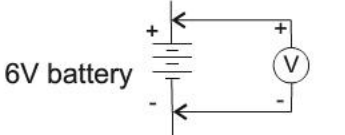
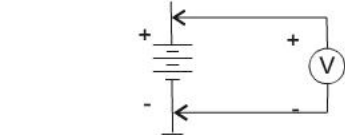
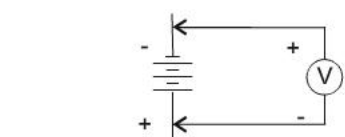
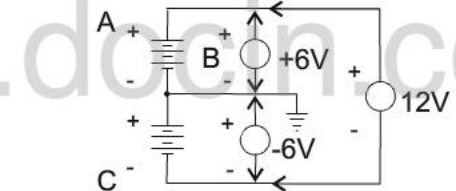
A. Voltage reading without ground	 <p>Voltmeter indicates 6V It is neither + nor -</p>
B. Negative terminal grounded	 <p>Voltmeter indicates +6V</p>
C. Positive terminal grounded	 <p>Voltmeter indicates -6V</p>
D. Placement of ground provides both positive and negative voltage	

Figure 9-32 Significance of zero reference point

COPYRIGHT © (2001) EATON CORPORATION

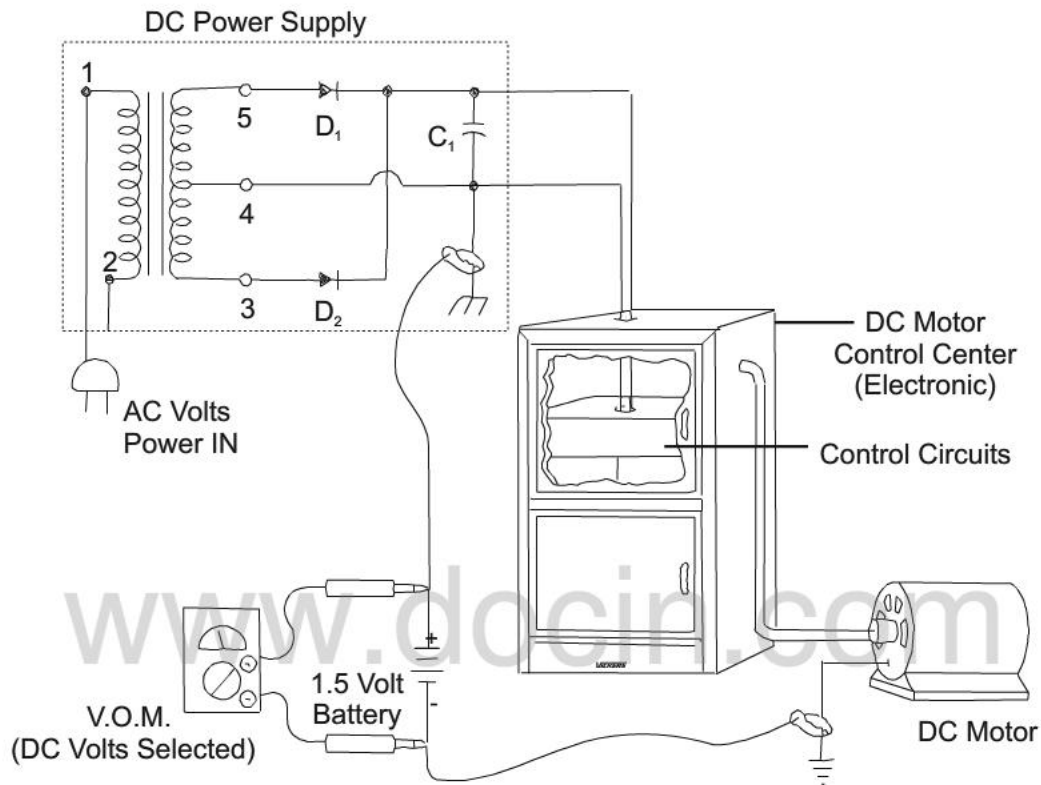


Figure 9-33 Testing for inadvertent connection of earth ground and chassis ground

COPYRIGHT © (2001) EATON CORPORATION

100999


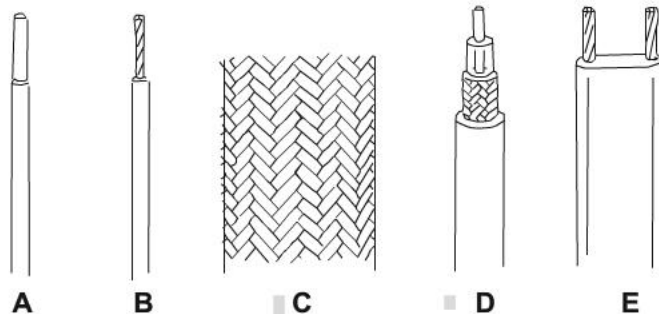
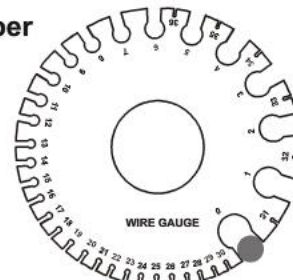


Figure 9-34 Common types of conductors

COPYRIGHT © (2001) EATON CORPORATION

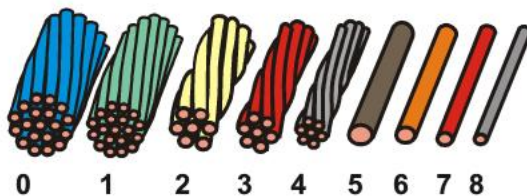B. Relationship between Wire Size and Gauge Number



C. American Wire Gauge (AWG)

Figure 9-35 Wire gauge numbers - characteristics and measurements

COPYRIGHT © (2001) EATON CORPORATION

A Wire Gauge Numbers and Characteristics

Gauge Number	Diameter (mils)	Area	Ohms per 1000 ft	Gauge Number	Diameter (mils)	Area	Ohms per 1000 ft
		Circular mils	25 deg C. Mils			Circular mils	25 deg. C mils
0000	460.0	212,000.0	0.0500	19	36.0	1,290.0	8.21
000	410.0	168,000.0	.0630	20	32.0	1,020.0	10.4
00	365.0	133,000.0	.0795	21	28.5	810.0	13.1
0	325.0	106,000.0	.100	22	25.3	642.0	16.5
1	289.0	87,700.0	.126	23	22.6	509.0	20.8
2	258.0	66,400.0	.159	24	20.1	404.0	26.2
3	229.0	52,600.0	.201	25	17.9	320.0	33.0
4	204.0	41,700.0	.253	26	15.9	254.0	41.6
5	182.0	33,100.0	.319	27	14.2	202.0	52.5
6	162.0	26,300.0	.403	28	12.6	160.0	66.2
7	144.0	20,800.0	.508	29	11.3	127.0	83.4
8	128.0	16,500.0	.641	30	10.0	101.0	105.0
9	114.0	13,100.0	.808	31	8.9	79.7	133.0
10	102.0	10,400.0	1.02	32	8.0	63.2	167.0
11	91.0	8,230.0	1.28	33	7.1	50.1	211.0
12	81.0	6,530.0	1.62	34	6.3	39.8	266.0
13	72.0	5,180.0	2.04	35	5.6	31.5	335.0
14	64.0	4,110.0	2.58	36	5.0	25.0	423.0
15	57.0	3,260.0	3.25	37	4.5	19.8	533.0
16	51.0	2,580.0	4.09	38	4.0	15.7	673.0
17	45.0	2,050.0	5.16	39	3.6	12.5	848.0
18	40.0	1,620.0	6.51	40	3.1	9.9	1,070.0

Figure 9.35A Wire Gauge Numbers and Characteristics




A. Nonmetallic sheathed cable	<div data-bbox="762 407 1166 463"> Type NM - 12-2  </div>
B. Armored cable consists of two or more insulated wires protected by a flexible metal cover	<div data-bbox="619 508 735 567">Insulated Wires</div> <div data-bbox="759 484 1161 564">  </div> <div data-bbox="1185 508 1361 567">Metal Flexible Cover</div>
C. Flexible cord is very tough and durable	<div data-bbox="767 724 1174 771">  </div> <div data-bbox="1294 765 1370 783">VICKERS</div>

Figure 9-36 Types of cable

COPYRIGHT © (2001) EATON CORPORATION

WIRE SIZE	In conduit, cable, or buried directly in the earth		Single conductors in free air		
	Types T, TW	Types RH RHW, THW	Types T, TW	Types RH RHW, THW	Weatherproof
	A	B	C	D	E
14	15	15	20	20	30
12	20	20	25	25	40
10	30	30	40	40	55
8	40	45	55	65	70
6	55	65	80	95	100
4	70	85	105	125	130
2	95	155	140	170	175
1/0	125	150	195	230	235
2/0	165	175	225	265	275
3/0	195	200	260	310	320

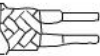Figure 9-37 Ampacity of copper wires

COPYRIGHT © (2001) EATON CORPORATION


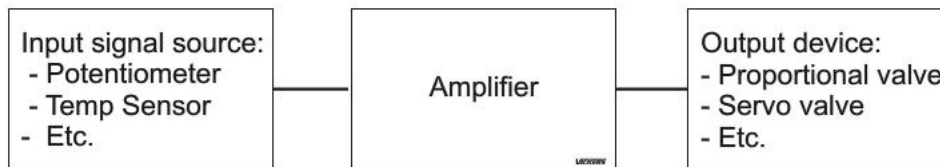


Figure 9-38 Functional block diagram of input device, amplifier and output device

COPYRIGHT © (2001) EATON CORPORATION

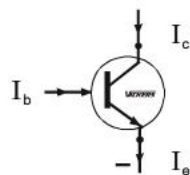

I_b (mA)	I_c (mA)	I_e (mA)
0	0	0
0.5	50	50.5
1	100	101
1.5	150	151.5

Figure 9-39 Schematic symbol and characteristics for a transistor

COPYRIGHT © (2001) EATON CORPORATION

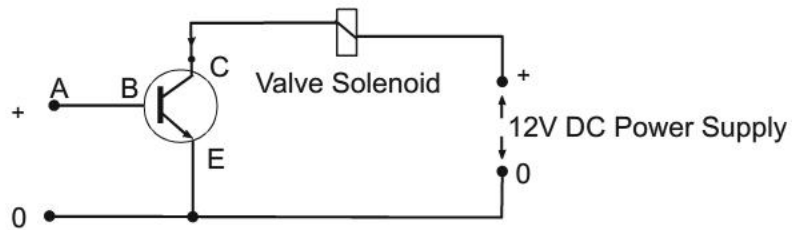


Figure 9-40 Amplifier circuit

COPYRIGHT © (2001) EATON CORPORATION



Figure 9-41 Stages of amplification

COPYRIGHT © (2001) EATON CORPORATION

www.docin.com

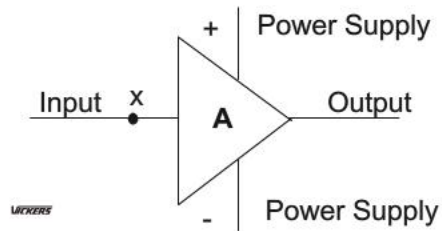


Figure 9-42 Schematic symbol for an amplifier card

COPYRIGHT © (2001) EATON CORPORATION

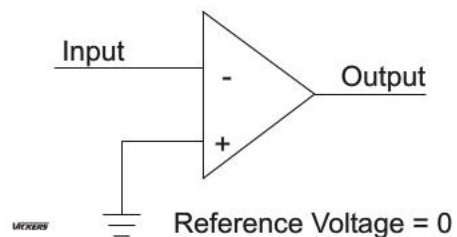


Figure 9-43 Amplifier with grounded input terminal for zero reference

COPYRIGHT © (2001) EATON CORPORATION

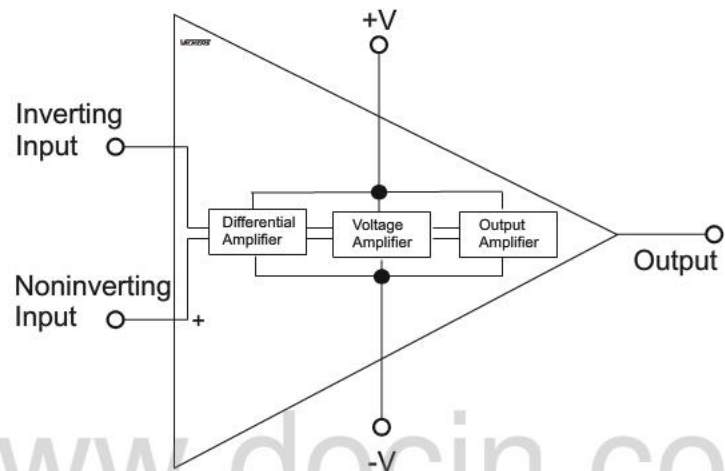


Figure 9-44 Basic operational amplifier

COPYRIGHT © (2001) EATON CORPORATION

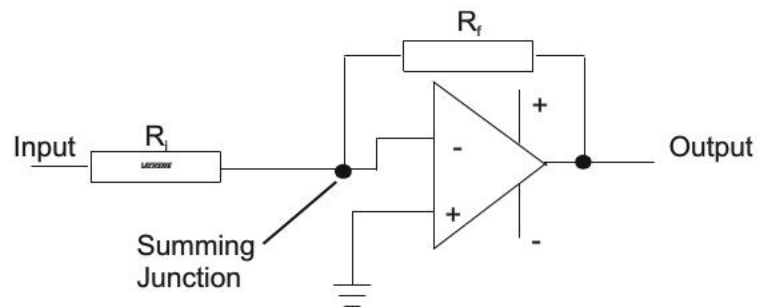


Figure 9-45 Typical Op Amp connections

COPYRIGHT © (2001) EATON CORPORATION

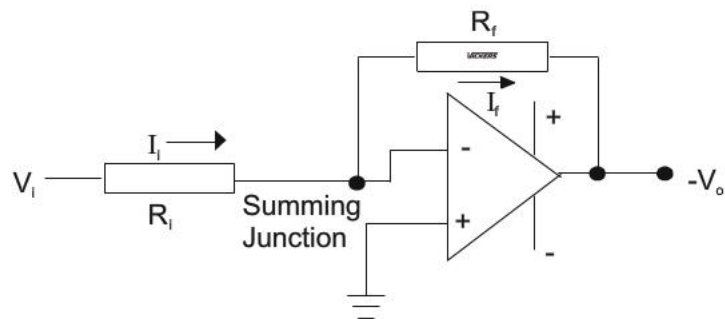


Figure 9-46 Typical Op Amp with voltage applied to input

COPYRIGHT © (2001) EATON CORPORATION

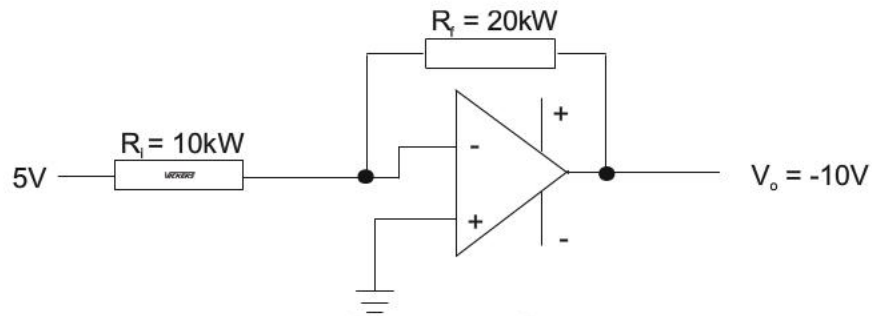


Figure 9-47 Example inverting amplifier circuit

COPYRIGHT © (2001) EATON CORPORATION

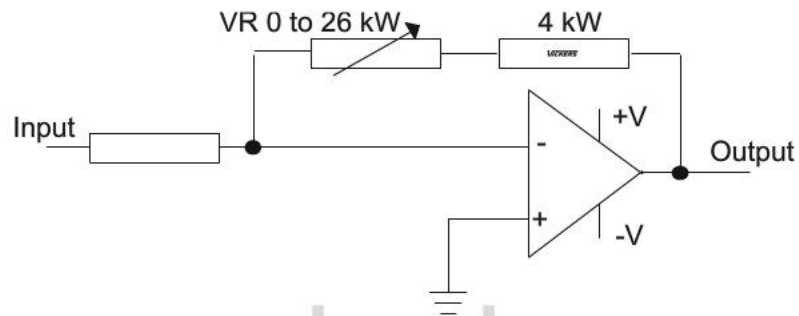


Figure 9-48 Op Amp with variable gain

COPYRIGHT © (2001) EATON CORPORATION

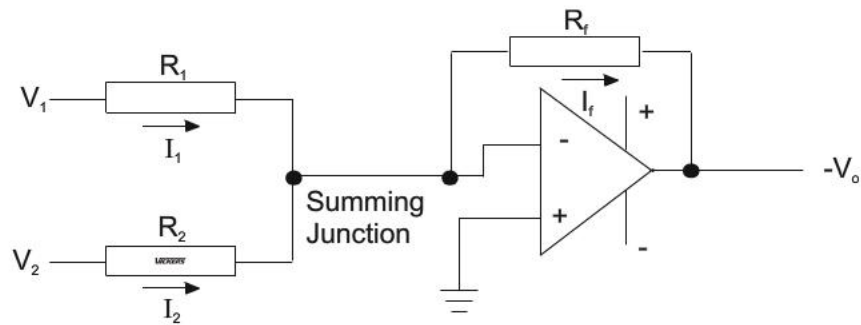


Figure 9-49 Op Amp with two inputs at the summing junction

COPYRIGHT © (2001) EATON CORPORATION

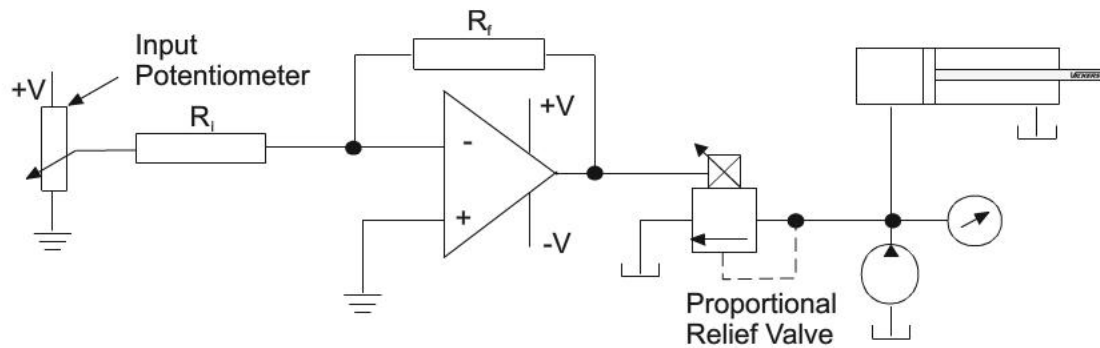


Figure 9-50 Pressure control circuit with op Amp including input potentiometer

COPYRIGHT © (2001) EATON CORPORATION

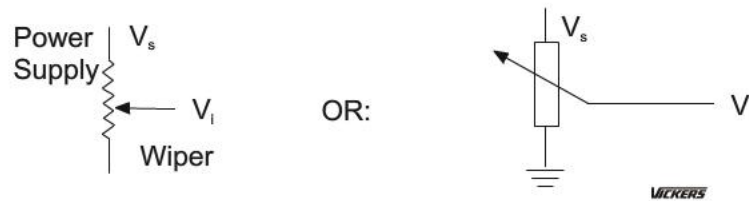


Figure 9-51 Potentiometer as a voltage divider

COPYRIGHT © (2001) EATON CORPORATION

www.docin.com

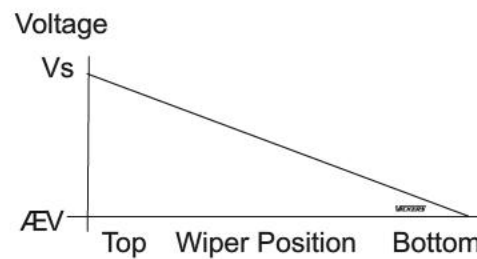


Figure 9-52 Linear relationship between wiper position and wiper voltage

COPYRIGHT © (2001) EATON CORPORATION

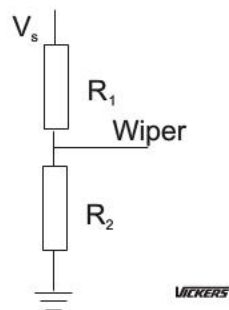


Figure 9-53 Potentiometer shown as two series resistor

COPYRIGHT © (2001) EATON CORPORATION


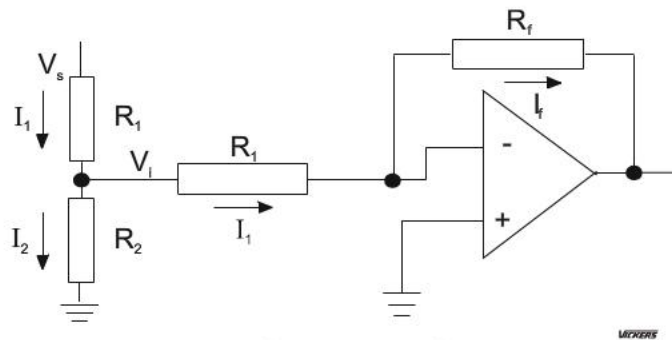


Figure 9-54 Potentiometer used to vary the input voltage

COPYRIGHT © (2001) EATON CORPORATION

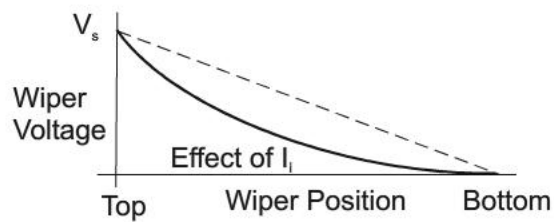

14000000

Figure 9-55 Nonlinear relationship between wiper position and wiper voltage

COPYRIGHT © (2001) EATON CORPORATION

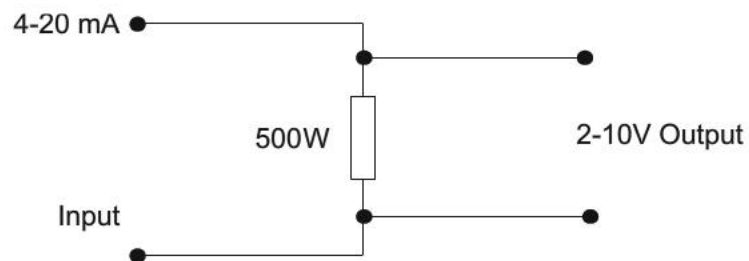


Figure 9-56 Circuit for converting a current signal to a voltage signal

COPYRIGHT © (2001) EATON CORPORATION

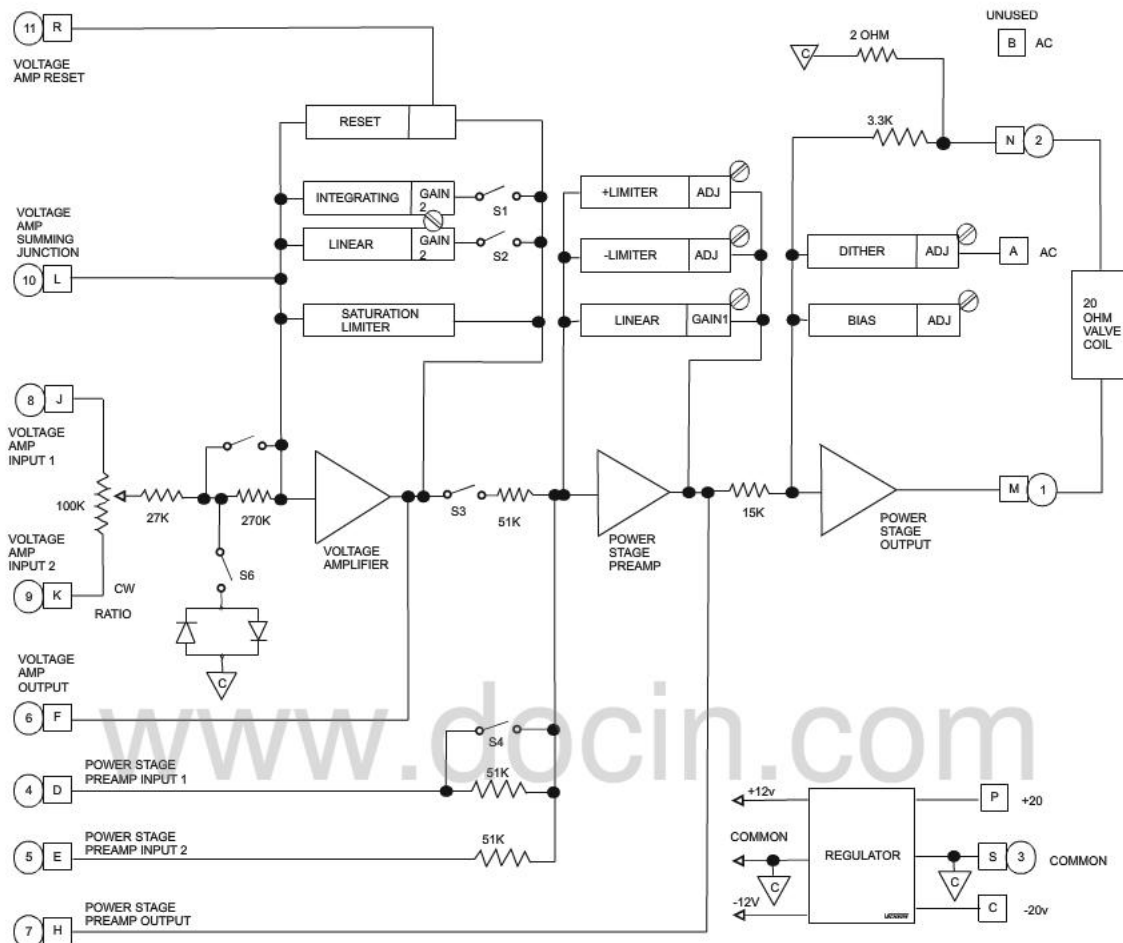


Figure 9-57 Typical industrial amplifier control module

COPYRIGHT © (2001) EATON CORPORATION

